



**Santa Clara
University**

COEN 210


Chapter 3— Part 2. Arithmetic for Computers

Yan Cui

ycui4@scu.edu

Arithmetic Circuits

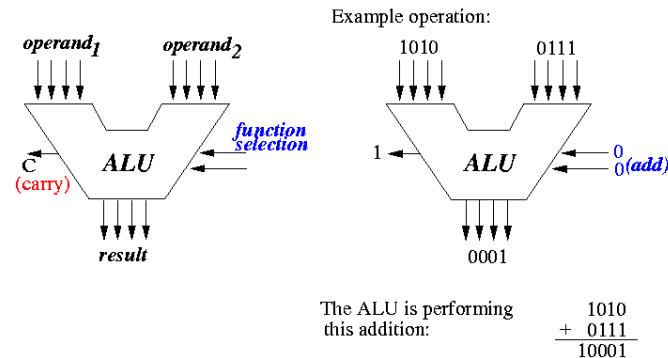- ▶ Arithmetic circuits perform basic arithmetic operations
 - ▶ Such as addition, subtraction and etc.
- ▶ They join together and form a **Arithmetic Logic Unit (ALU)**
 - ▶ Like a Swiss army knife, single unit perform multiple arithmetic and logical operations




- ▶ An **ALU** is the part of a computer processor(CPU) that carries out **arithmetic and logic operations** on the operands in computer instruction words.

Combinational Circuits


What is a Combinational Circuit

 - ▶ Consists of an **acyclic** network of logic gates
 - ▶ Continuously responds to changes in inputs
 - ▶ Outputs become (after a short delay) boolean functions of the inputs.
 - ▶ memoryless digital logic circuits
 - ▶ whose output at any instant in time depends only on the combination of its inputs




Three ways for a combinational logic circuit

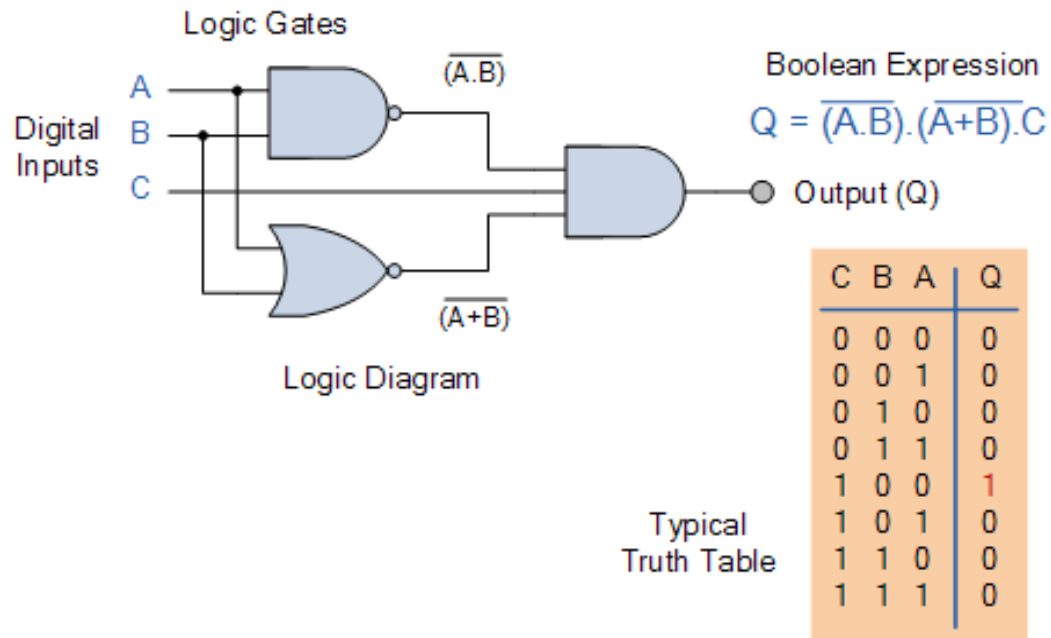- ▶ Boolean Algebra
- ▶ Truth Table
- ▶ Logic Diagram



Classification of Combinational Logic

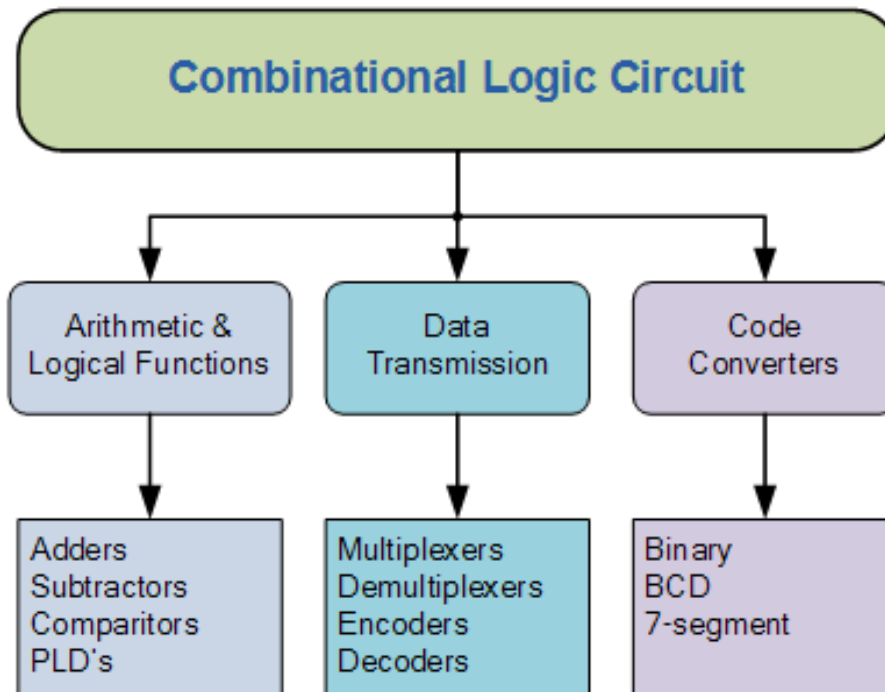Multiplexers, Decoders, Full and Half Adders, Comparators, etc.





Addition & Subtraction

Single-Bit Half Adder

- ▶ Input : single bit **A** and **B**
- ▶ Output: single bit Sum **S** and Carry **C**

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1


Truth table

  

Single Bit Full Adder


- ▶ same as half adder except it has an **carry input**
- ▶ Output: sum and carry output

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Cin: carry input
Cout: carry output


Adding a Pair of 4-bit Integers

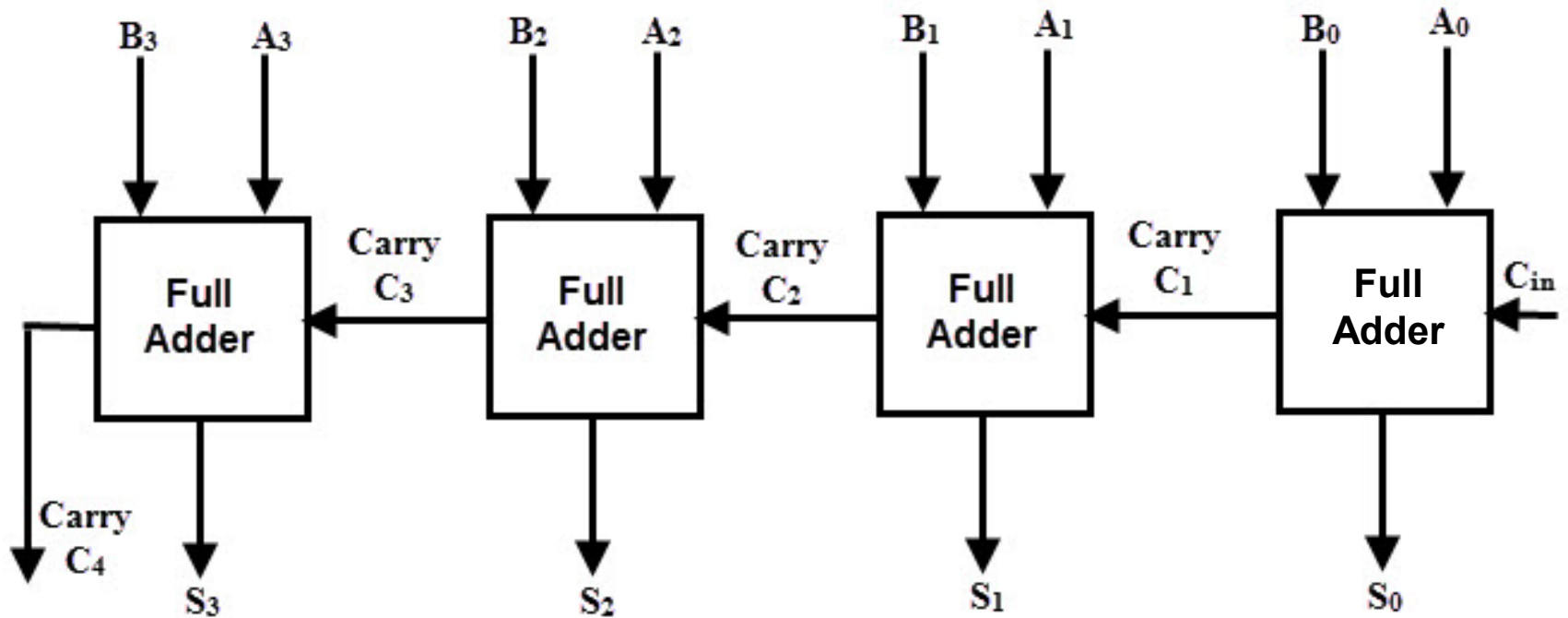

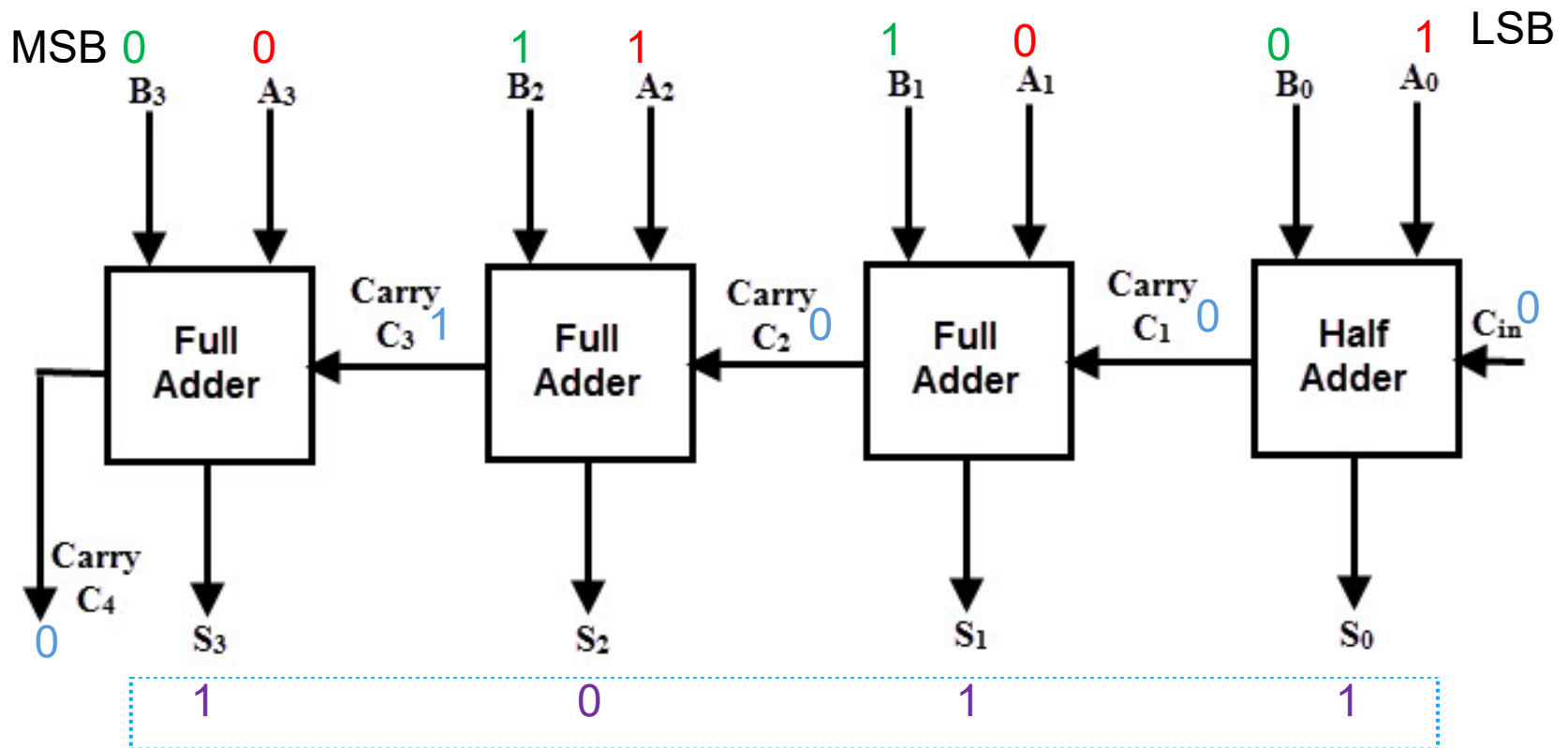Example:

Let $A = 0101_2$ and $B = 0110_2$, What is $A + B$?


- ▶ A0 – A3 1st 4-bit number 0 1 0 1₂
- ▶ B0 – B3 2nd 4-bit number 0 1 1 0₂
- ▶ A + B ?



How about Subtraction?

► $-B = \bar{B} + 1 \rightarrow A - B = A + \bar{B} + 1$

► $S=1 \rightarrow$ subtraction

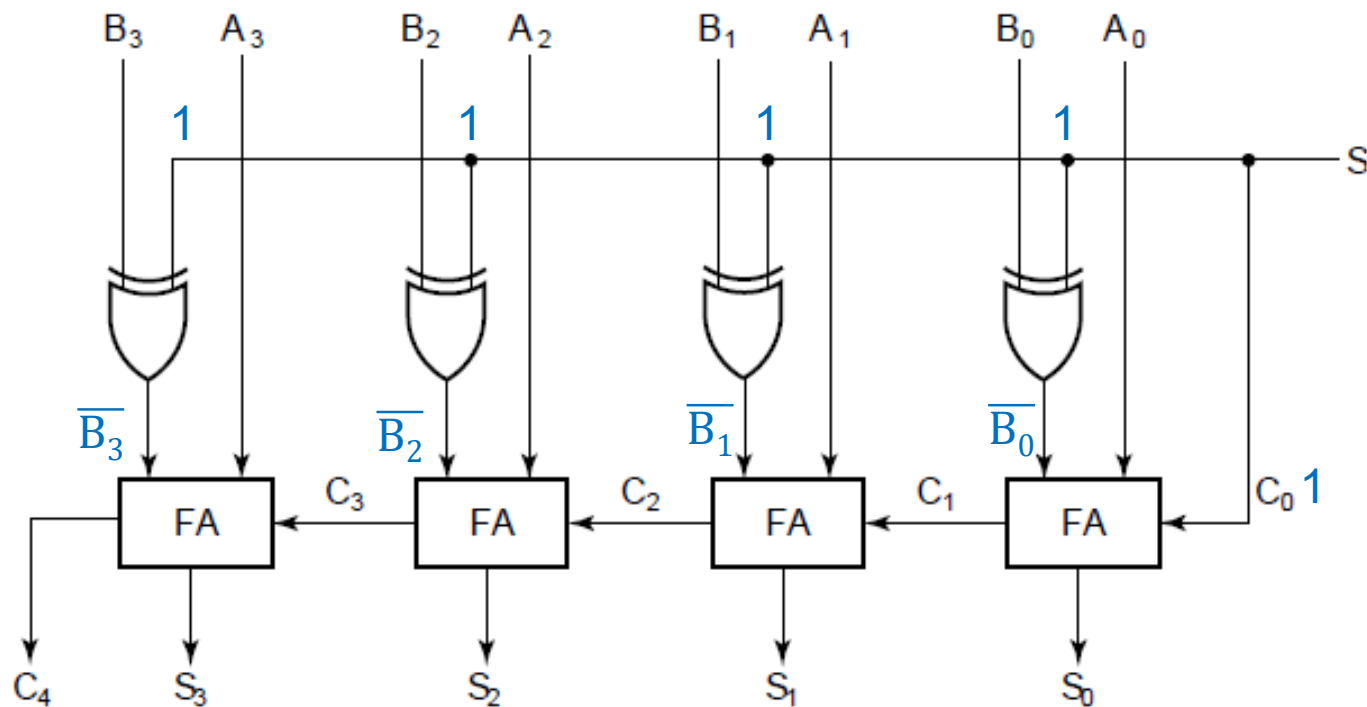

Overflow

Preface

- ▶ "Overflow" is only meaning for systems with fixed number of digits
 - ▶ E.g, computers
 - ▶ Overflow occurs when there are insufficient bits in a binary number representation to portray the result of an arithmetic operation
 - ▶ Overflow can apply to both signed and unsigned
-

Overflow Summary - Addition for Signed Number

- ▶ Adding a positive operand and a negative operand, no overflow
 - ▶ Adding two positive operands
 - ▶ Overflow if result is negative (i.e., sign bit is 1)
 - ▶ Adding two negative operands
 - ▶ Overflow if result is positive (i.e., sign bit is 0)
-

Overflow Examples – Addition of Signed Number

Overflow!

$$\begin{array}{r} 0011 \quad 3 \\ + 0110 \quad 6 \\ \hline 1001 \quad -7 \end{array}$$

OK!

$$\begin{array}{r} 1101 \quad -3 \\ + 0110 \quad 6 \\ \hline 0011 \quad 3 \end{array}$$

OK!

$$\begin{array}{r} 1011 \quad -5 \\ + 1110 \quad -2 \\ \hline 1001 \quad -7 \end{array}$$

Overflow!

$$\begin{array}{r} 1001 \quad -7 \\ + 1000 \quad -8 \\ \hline 0001 \quad 1 \end{array}$$

Overflow Summary – Subtraction for Signed Number

- ▶ Subtracting between two positive or two negative operands
 - ▶ no overflow
 - ▶ Subtracting a positive operand from a negative operand
 - ▶ Overflow if result is positive (i.e., result sign bit is 0)
 - ▶ Subtracting a negative operand from a positive operand
 - ▶ Overflow if result is negative (i.e., sign bit is 1)
-

Overflow Examples – Subtract for Signed Number

OK!

$$\begin{array}{r} 0011 \quad 3 \\ - 0110 \quad 6 \\ \hline 0011 \\ 1001 \\ + \quad 1 \\ \hline 1101 \quad -3 \end{array}$$

Overflow!

$$\begin{array}{r} 1101 \quad -5 \\ - 0110 \quad 6 \\ \hline 1101 \\ 1001 \\ + \quad 1 \\ \hline 0111 \quad 7 \end{array}$$

OK!

$$\begin{array}{r} 1011 \quad -5 \\ - 1110 \quad -2 \\ \hline 1011 \\ 0001 \\ + \quad 1 \\ \hline 1101 \quad -3 \end{array}$$

Overflow!

$$\begin{array}{r} 0001 \quad 1 \\ - 1000 \quad -8 \\ \hline 0001 \\ 0111 \\ + \quad 1 \\ \hline 1001 \quad -7 \end{array}$$

How about Unsigned Numbers?


- ▶ For addition,
 - ▶ Overflow happens when carry bit is 1
 - ▶ For subtraction
 - ▶ Underflow happens when first operand is less than second operand
 - ▶ In RISC-V
 - ▶ No overflow detection
 - ▶ No special instruction set support for overflow checks on base instruction sets
 - Some overflow checks can be implemented using RISC-V branches
 - E.g. unsigned addition, `add t0, t1, t2; bltu t0, t1, overflow.`
 - ▶ Floating point generate a exception
-

Dealing with Overflow in High-Level Languages

- ▶ Some languages (e.g., C and Java) ignore overflow
 - ▶ So C compiler always use MIPS `addu`, `addui`, `subu` instructions, even for signed variables
- ▶ Other languages (e.g., Ada, Fortran) require raising an exception

One-bit Equality Comparator

 - ▶ Output 1 when both bits are same
 - ▶ $C = (A * B) \vee (A' * B')$
 - ▶ When $A = B$, either $A = B = 1$ (HIGH) or $A = B = 0$ (LOW)
- ▶ *Can it be simpler?*




One-Bit Equality Comparator

- ▶ Output 1 when both bits are same

- ▶ $C = (A * B) \vee (A' * B')$


- ▶ *Can it be simpler?*

- ▶ *XNOR gate*

 



Four Bit Equality Comparator

 - ▶ The circuit of the equality comparator consists of an exclusive NOR gate ([XNOR](#)) per pair of input bits. If the two inputs are identical (both 1s or both 0s) an output of logic 1 is obtained.
- ▶ The outputs of the XNOR gates are then combined in an [AND gate](#), the output of which will be 1, only when all the XNOR gates indicate matched inputs.




Word Comparator

- ▶ Assume 32bit word

  

Magnitude Comparators

 - ▶ Indicate equality $A = B$, A is greater than B ($A > B$), A is less than B ($A < B$)
- ▶ A simple 1-bit magnitude comparator is shown in figure
 - ▶ Gate 1 produces the function $A > B$
 - ▶ gate 3 gives $A < B$
 - ▶ gate 2 is an XNOR gate giving an equality output.



A simple 1-bit magnitude comparator


Comparator Truth Table

Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Multiplexer


- ▶ *selects* one of several input signals and passes it on to the output
 - ▶ A combinational logic circuit
 - ▶ Also known as the “selector” circuit
 - ▶ **Selection** is controlled by a particular set of input lines whose # depends on the # of the data input lines.
 - ▶ For a 2^n -to-1 multiplexer, there are 2^n data input lines and n selection lines whose bit combination determines which input is selected.
 - ▶ shortened to “MUX” or “MPX”
-

Multiplexer (Cont.)

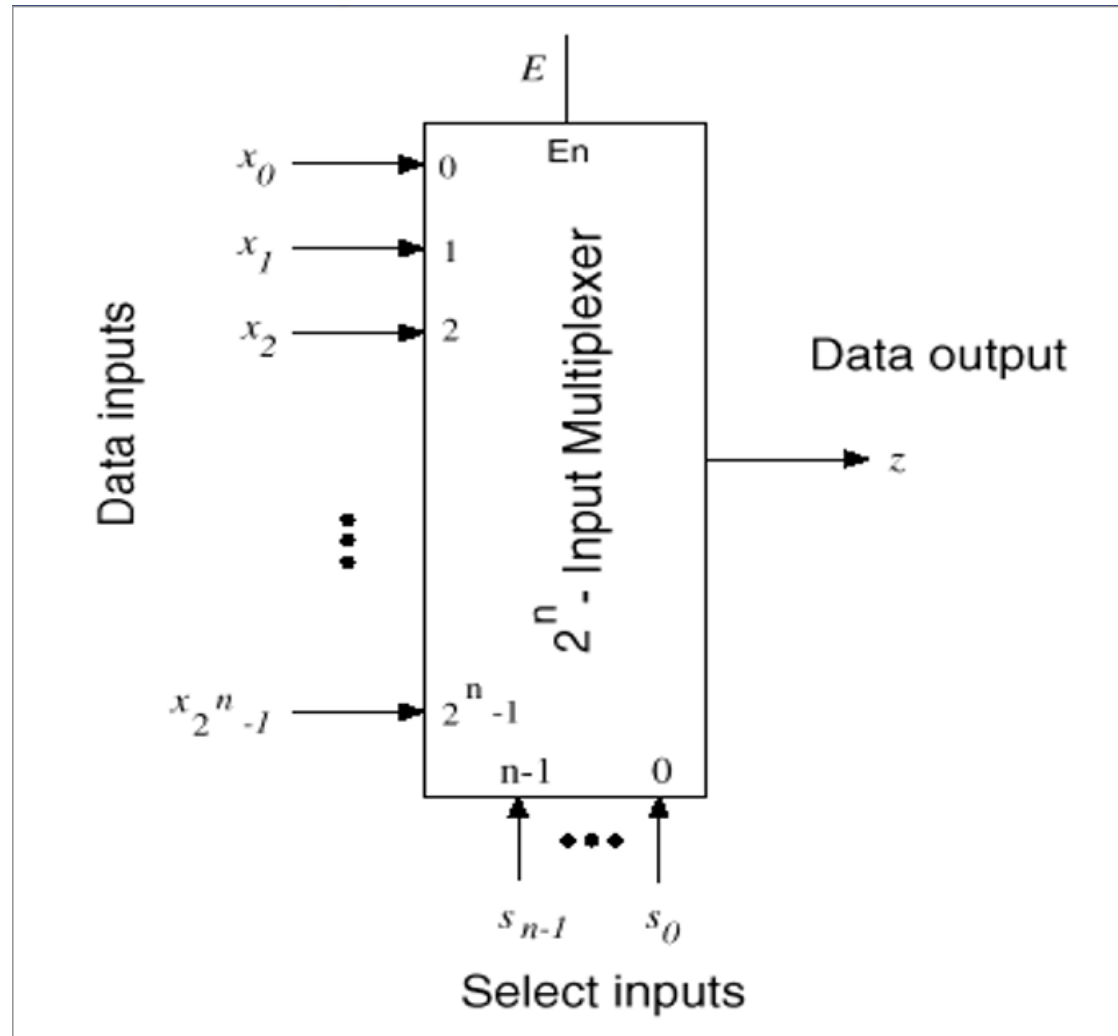


 
Example: 2-to-1-Line Multiplexer

- ▶ Since $2 = 2^1$, $n = 1$
- ▶ The single selection variable S has two values:
 - ▶ $S = 0$ selects input I_0 Out = I_0
 - ▶ $S = 1$ selects input I_1 Out = I_1
- ▶ The circuit:




Word Multiplexer

  - ▶ Output word A when $S == 1$
 - ▶ A: 32-bit word $a_{31} a_{30} a_{29} \dots a_1 a_0$
- ▶ Output word B when $S == 0$
 - ▶ B: 32-bit word $b_{31} b_{30} b_{29} \dots b_1 b_0$



 Example: 4-to-1 MUX

- ▶ Since $4 = 2^2$, $n = 2$
- ▶ The two selection variable S_0, S_1 has four values:
 - ▶ $S_1 = 0, S_0 = 0$ selects input D_0 , $Y = D_0$
 - ▶ $S_1 = 0, S_0 = 1$ selects input D_1 , $Y = D_1$
 - ▶ $S_1 = 1, S_0 = 0$ selects input D_2 , $Y = D_2$
 - ▶ $S_1 = 1, S_0 = 1$ selects input D_3 , $Y = D_3$
- ▶ The circuit:




Binary Decoder

- ▶ A combinational circuit that converts binary information from n coded inputs to a maximum 2^n coded outputs
 - ▶ Accepts a set of inputs that represents a binary number and activates only the output that corresponds to that input number.
 - ▶ n -to- 2^n decoder
 - ▶ Only 1 output is asserted for each input combination
 - ▶ Translates the n -bit input into a signal that corresponds to the binary value
 - ▶ Transforms n -bit input signals into an equivalent code using 2^n outputs.
-

 Example: 2-to-4 Binary Decoder

- ▶ The **two input** lines are decoded into **four output** lines.
- ▶ Only one output line will be **active (logic 1)** and the other three output lines are maintained at **logic zero**



2 to 4 Decoder

Example: 2-to-4 Binary Decoder (Cont.)

▶ Truth Table:

Binary Value	A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	0	1
1	0	1	0	0	1	0
2	1	0	0	1	0	0
3	1	1	1	0	0	0

*Accepts a set of inputs that represents a binary number and **activates only the output that corresponds to that input number.***

- ▶ If the two inputs are both 0, then the output of D_0 is logic 1 and the other outputs are logic 0.
 - ▶ If both the inputs are 1, then the output of D_3 is logic 1 and other output pins are logic 0.
 - ▶ If the input pins $A_1 = 0$ & $A_0 = 1$ then the D_1 will be logic 1, other output are 0.
 - ▶ if the inputs $A_1 = 1$ & $A_0 = 0$ then the output D_2 will be logic 1, others are 0.
-

Example: 2-to-4 Binary Decoder (Cont.)

- ▶ Boolean expressions of each output:

Equations

$$D_0 = \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{A_1} \cdot A_0$$

$$D_2 = A_1 \cdot \overline{A_0}$$

$$D_3 = A_1 \cdot A_0$$

Example: 2-to-4 Binary Decoder (Cont.)

- ▶ By using the above equation, we can implement the logic circuit design:


Equations

$$D_0 = \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{A_1} \cdot A_0$$

$$D_2 = A_1 \cdot \overline{A_0}$$


$$D_3 = A_1 \cdot A_0$$

 

- ▶ There are two NOT gates and four AND gates are used.
- ▶ The output depends on the product of the two inputs

 Example: 3-to-8 Binary Decoder


- ▶ Each output can be implemented with a 3-input AND gate
- ▶ Our example would need 8 3-input AND gates



3-to-8 Decoder

Inputs			Outputs							
I2	I1	I0	O7	O6	O5	O4	O3	O2	O1	O0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Example: 3-to-8 Binary Decoder (Cont.)

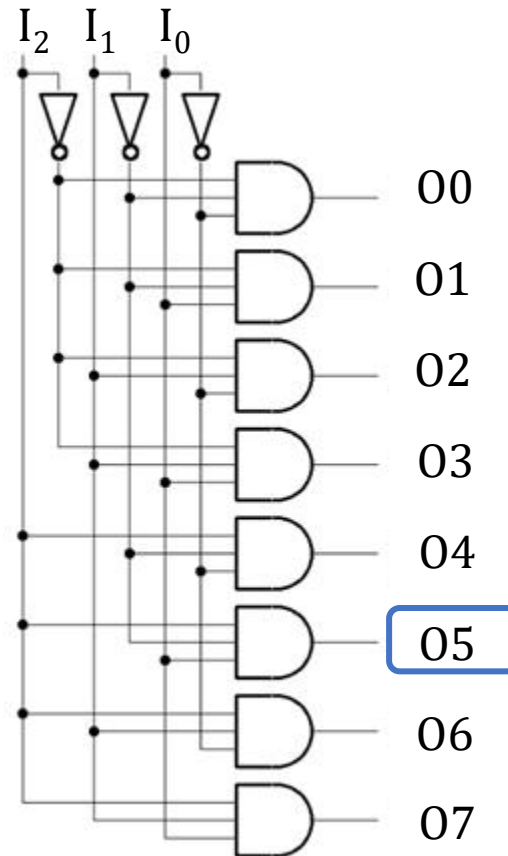

Logic Circuit


Arithmetic Logic Unit (ALU)

What is ALU?

- ▶ Perform arithmetic and bitwise operations on integer binary numbers
 - ▶ Multiple functions: add, subtract, and, xor, others
 - ▶ Combinational logic to perform functions.
 - ▶ Control signals select function to be performed.
 - ▶ Modular with multiple instances of 1-bit ALU
-

An Example of 4-bit ALU

 - ▶ Combination logic : continuously responding to inputs
- ▶ 3-bit control signal selects the operation
- ▶ In addition to output, also compute flags



Z, C and V are status flags


Z = 1 if F=0

C = Carry or Borrow

V = Overflow

S ₂	S ₁	S ₀	Function (F)
0	0	0	A+B
0	0	1	A-B
0	1	0	A-1
0	1	1	A+1
1	0	0	$A \wedge B$
1	0	1	$A \vee B$
1	1	0	NOT A
1	1	1	$A \oplus B$

An Example of 4-bit ALU

 

Z , C and V are status flags


$Z = 1$ if $F = 0$

C = Carry or Borrow

V = Overflow

S_2	S_1	S_0	Function (F)
0	0	0	$A + B$
0	0	1	$A - B$
0	1	0	$A - 1$
0	1	1	$A + 1$
1	0	0	$A \wedge B$
1	0	1	$A \vee B$
1	1	0	NOT A
1	1	1	$A \oplus B$

An Example of 4-bit ALU

 

Z, C and V are status flags

Z = 1 if $F=0$

C = Carry or Borrow

V = Overflow

S ₂	S ₁	S ₀	Function (F)
0	0	0	A+B
0	0	1	A-B
0	1	0	A-1
0	1	1	A+1
1	0	0	$A \wedge B$
1	0	1	$A \vee B$
1	1	0	NOT A
1	1	1	$A \oplus B$

Let Us Design a 32-bit ALU

▶ Inputs


- ▶ Two 32-bit binary values
- ▶ 3-bit control input, Op

▶ Outputs


- ▶ 32-bit calculated result, Out
- ▶ 1-bit output flag, Zero
 - ▶ Set to 1 if Out are all 0's
 - ▶ Useful for checking branch conditions (i.e. if (A == B))

▶ Functions

 
- ▶ 32-bit-wide arithmetic operations
 - ▶ Op == 000 : Out = A AND B
 - ▶ Op == 001 : Out = A OR B
 - ▶ Op == 010 : Out = A + B
 - ▶ Op == 110 : Out = A - B
-



... Which is 32 units of 1-bit ALU.

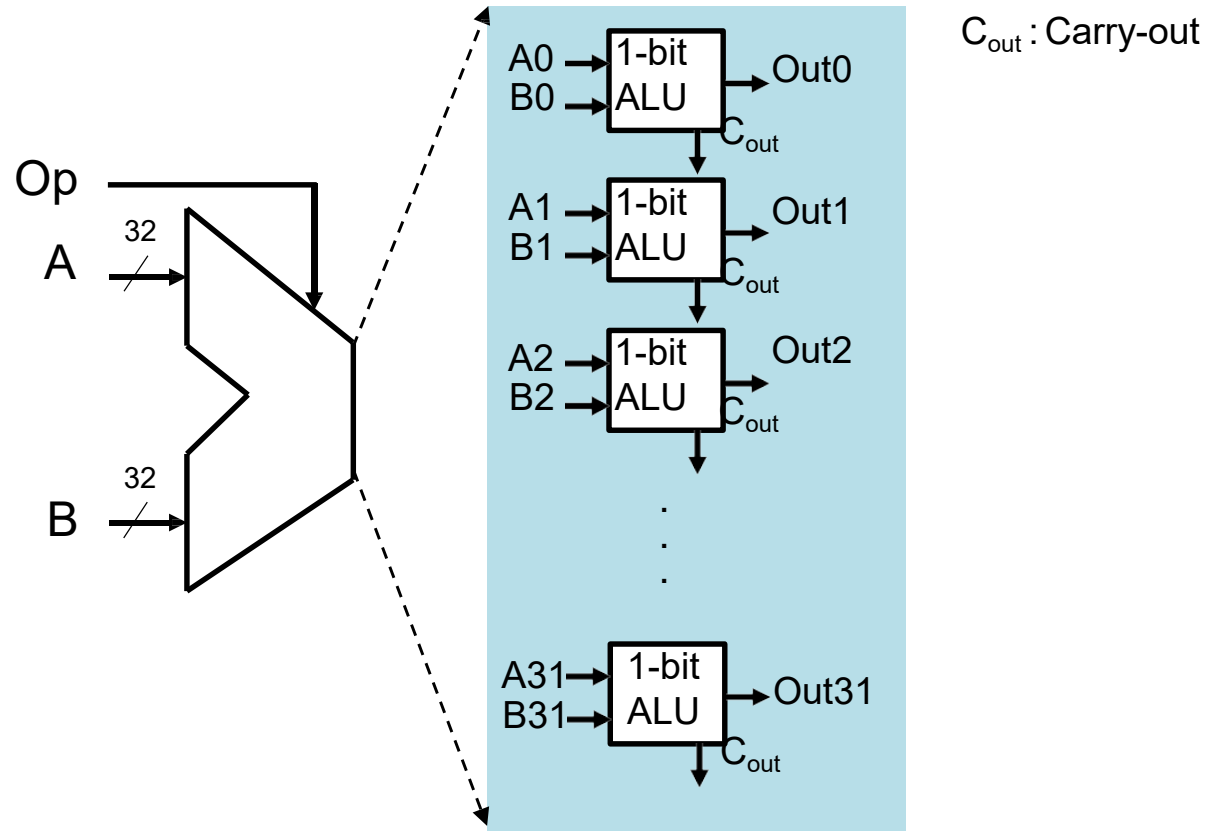


1-bit AND/OR ALU

 

If ($Op == 0$), $Out = A \text{ AND } B$


If ($Op == 1$), $Out = A \text{ OR } B$

Merge Full Adder

 

If (Op == 00), Out = A AND B
If (Op == 01), Out = A OR B
If (Op == 10), Out = A + B

Merge More Logics

 

If $(Op (Op_2Op_1Op_0) == 000)$, Out = A AND B


If $(Op (Op_2Op_1Op_0) == 001)$, Out = A OR B

If $(Op (Op_2Op_1Op_0) == 010)$, Out = A + B

If $(Op (Op_2Op_1Op_0) == 110)$, Out = A - B

Why designer choose subtract op to be 110?

 Merge More Logics – What if subtract is op 11?




If (Op (Op₂Op₁Op₀) == 000), Out = A AND B
If (Op (Op₂Op₁Op₀) == 001), Out = A OR B
If (Op (Op₂Op₁Op₀) == 010), Out = A + B
If (Op (Op₂Op₁Op₀) == 110), Out = A - B



If (Op (Op₁Op₀) == 00), Out = A AND B
If (Op (Op₁Op₀) == 01), Out = A OR B
If (Op (Op₁Op₀) == 10), Out = A + B
If (Op (Op₁Op₀) == 11), Out = A - B

What if we want subtraction to be Op = 11?

 
Improvement– What if subtract is op 11? (1)



If (Op (Op₁Op₀) == 00), Out = A AND B
If (Op (Op₁Op₀) == 01), Out = A OR B
If (Op (Op₁Op₀) == 10), Out = A + B
If (Op (Op₁Op₀) == 11), Out = A - B

Step1: AND gate of Op₀ and Op₁ to simulate Op₂


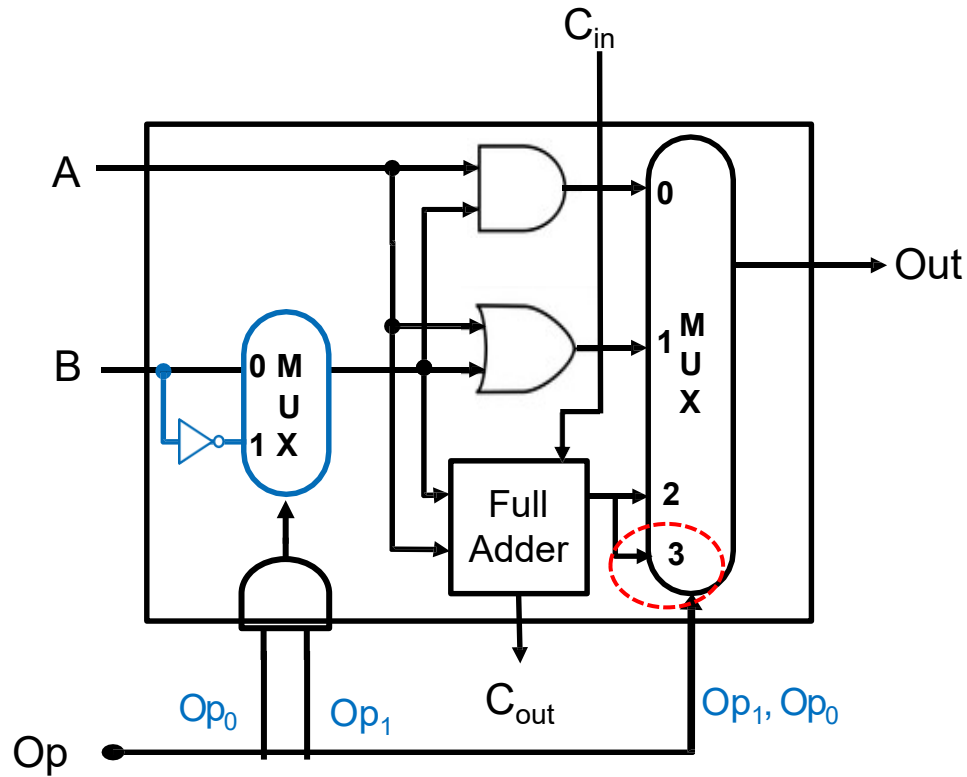
Improvement– What if subtract is op 11? (2)




If (Op ($Op_1 Op_0$) == 00), Out = A AND B
If (Op ($Op_1 Op_0$) == 01), Out = A OR B
If (Op ($Op_1 Op_0$) == 10), Out = A + B
If (**Op** ($Op_1 Op_0$) == **11**), Out = A – B

Step 2: Route full adder output to MUX input 3 as well

Put It Altogether

 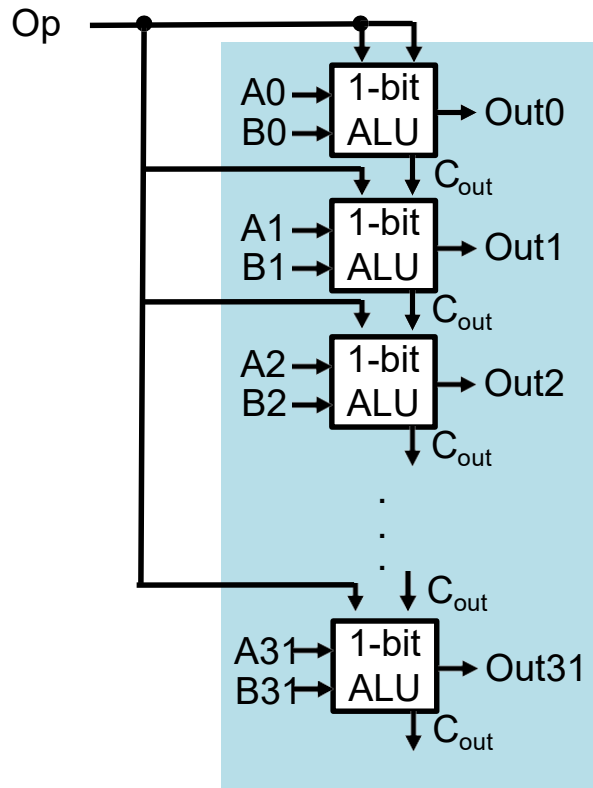

What about Zero Flag?

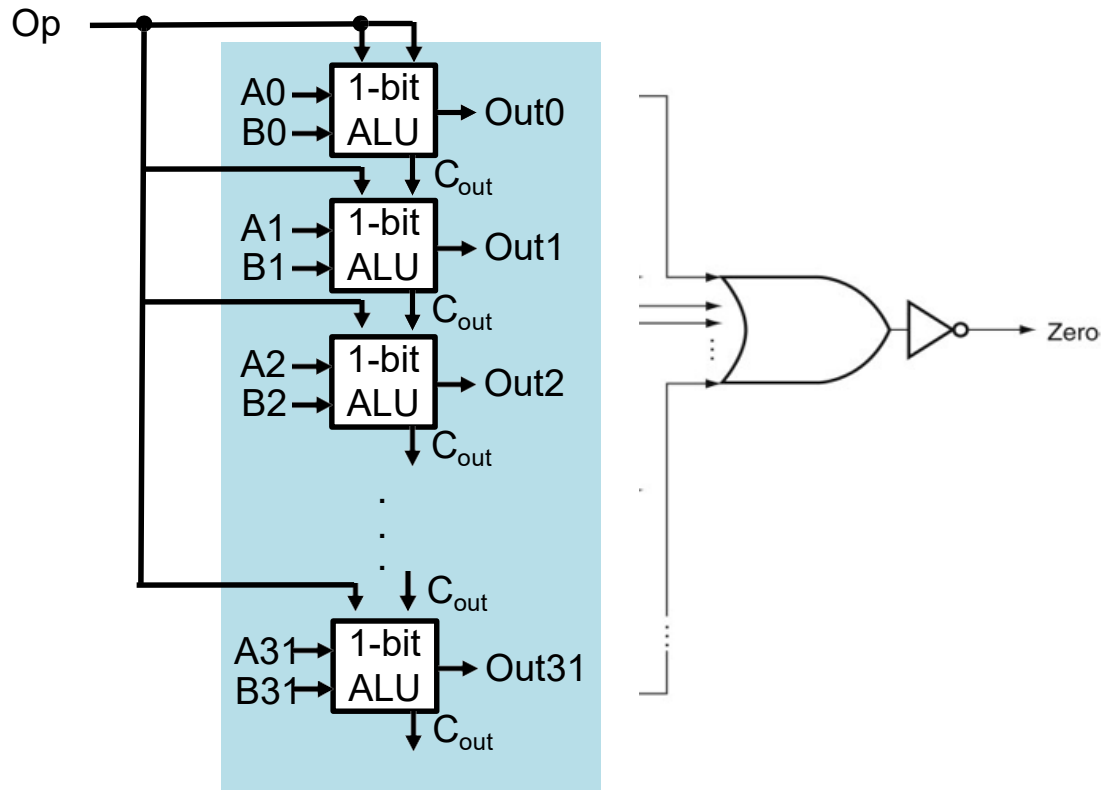

Multiplication

Multiplication – Learn from Paper-n-Pencil

Diagram illustrating the multiplication process:


multiplicand	→	1000
multiplier	×	1001

		1000
		0000
		0000
		1000
product	→	-----
		1001000



Length of product is
the sum of operand
lengths

Multiplication – Learn from Basics


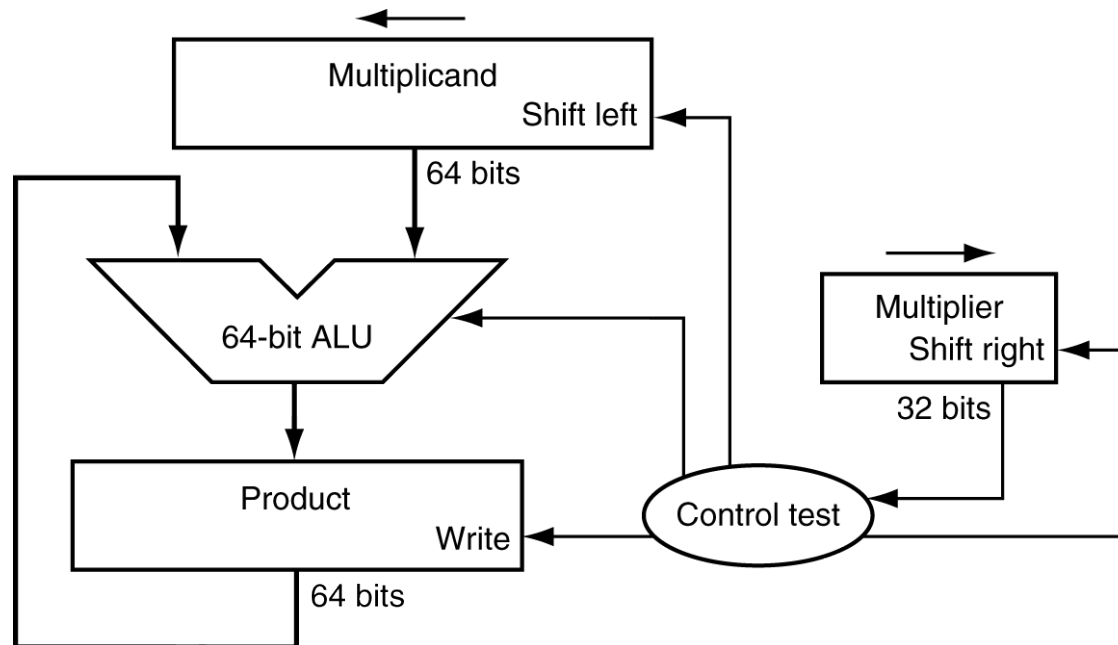
- ▶ Long-multiplication approach
 - ▶ Iterative addition of shifted multiplicands





Multiplication Hardware

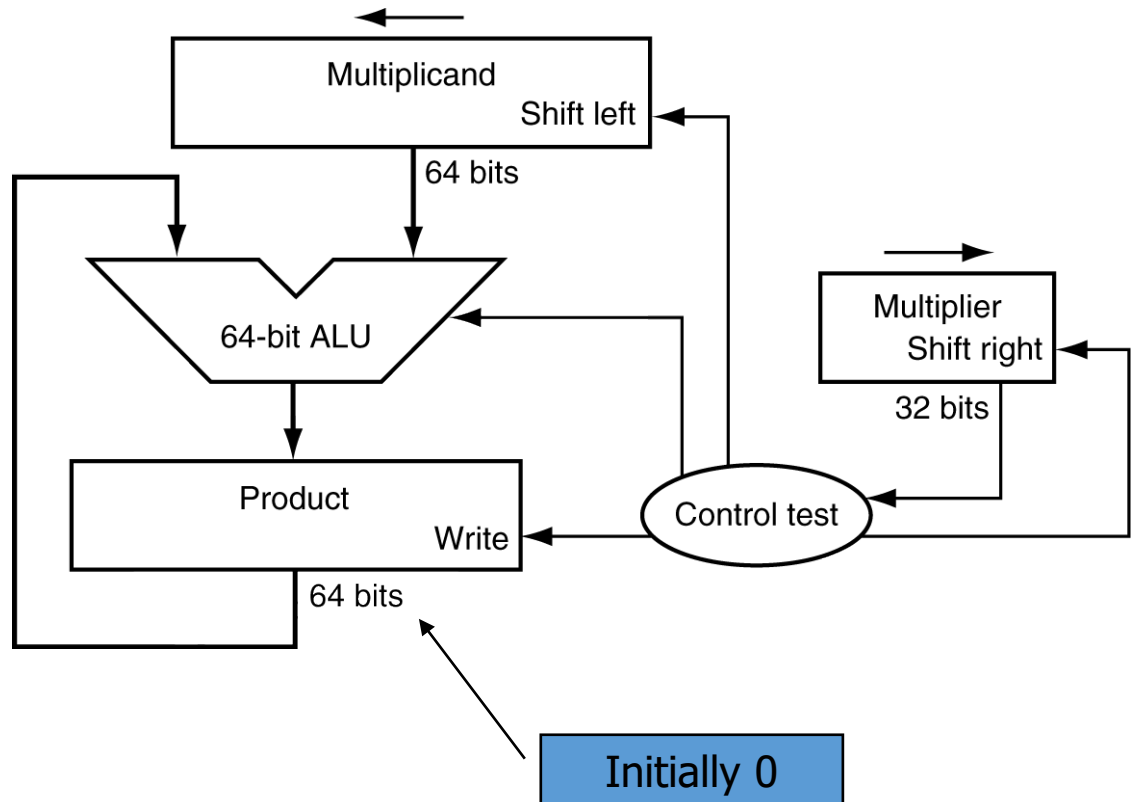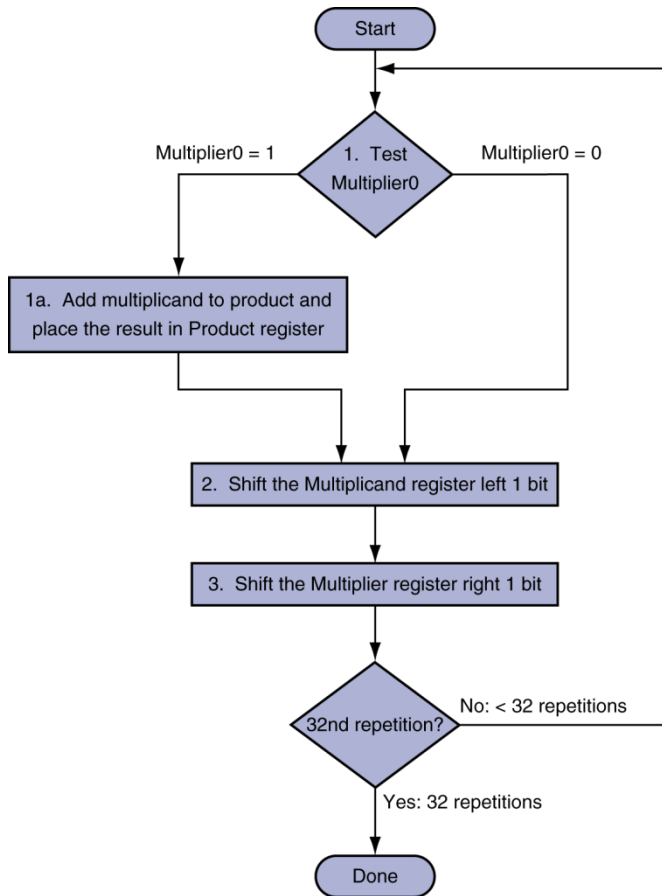

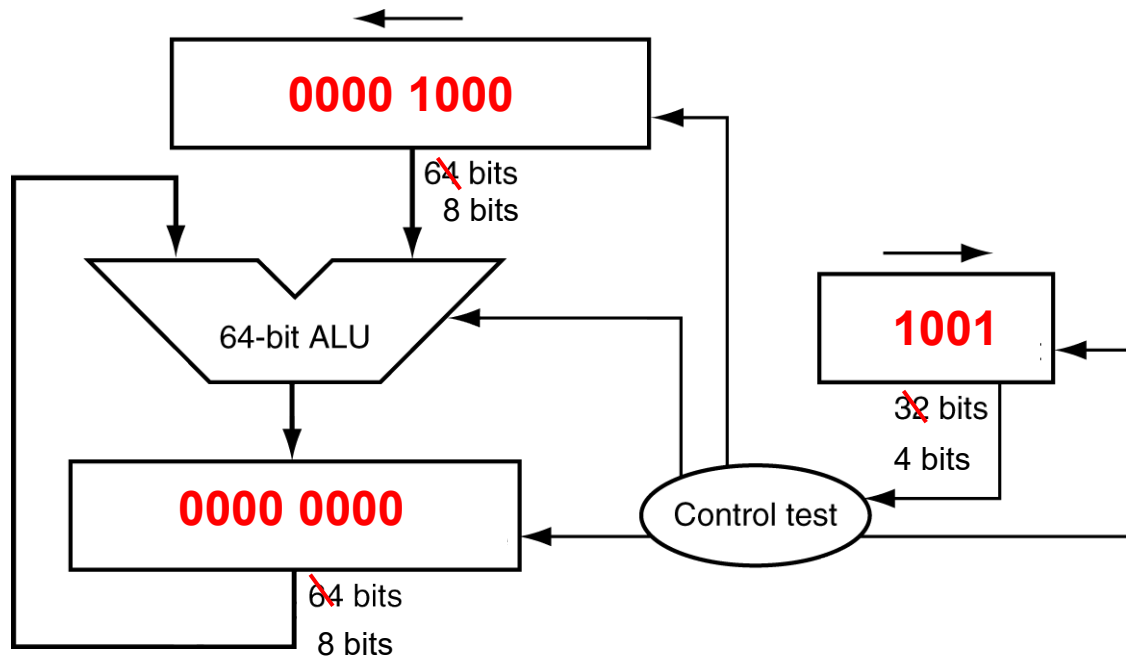
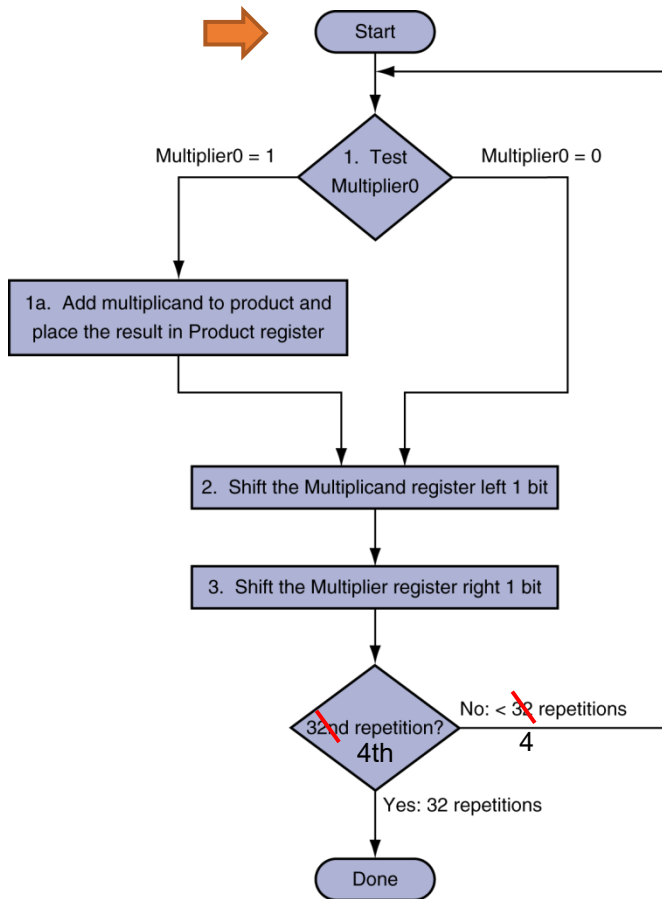
Multiplication Example, 8 x 9 or 1000 x 1001 – Start



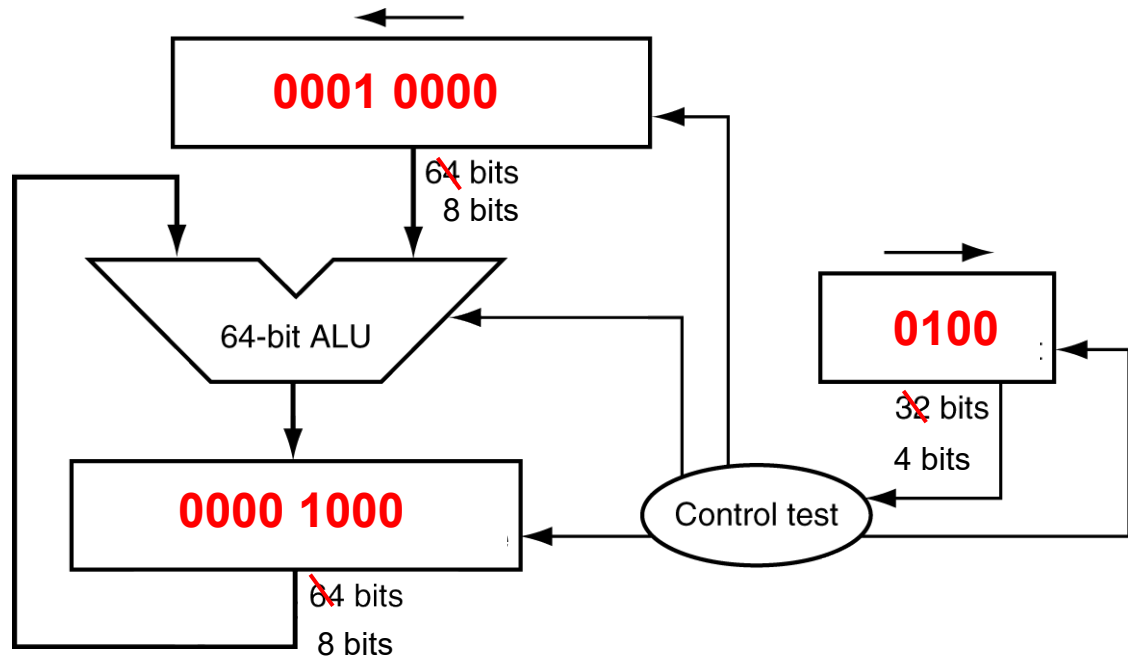
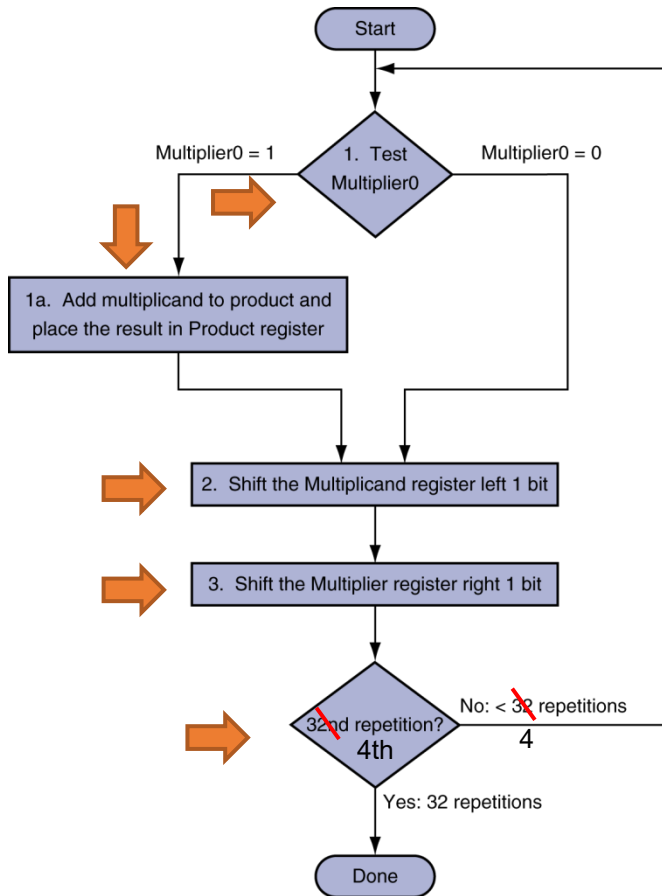
Multiplication Example, 1000 x 1001 – Iteration 1



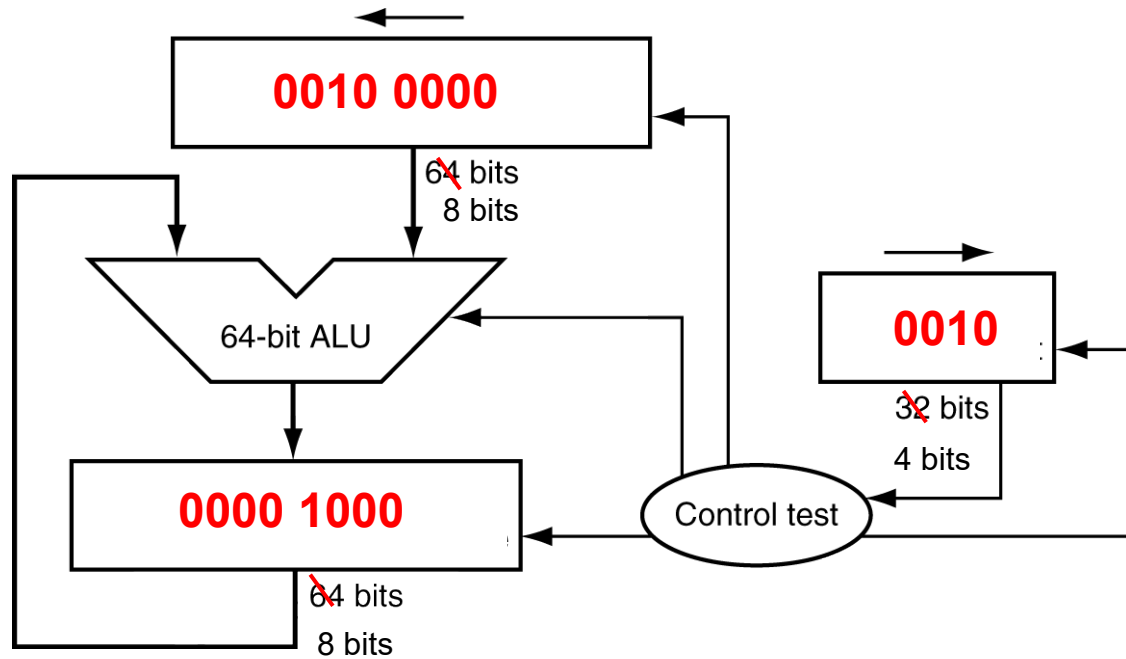
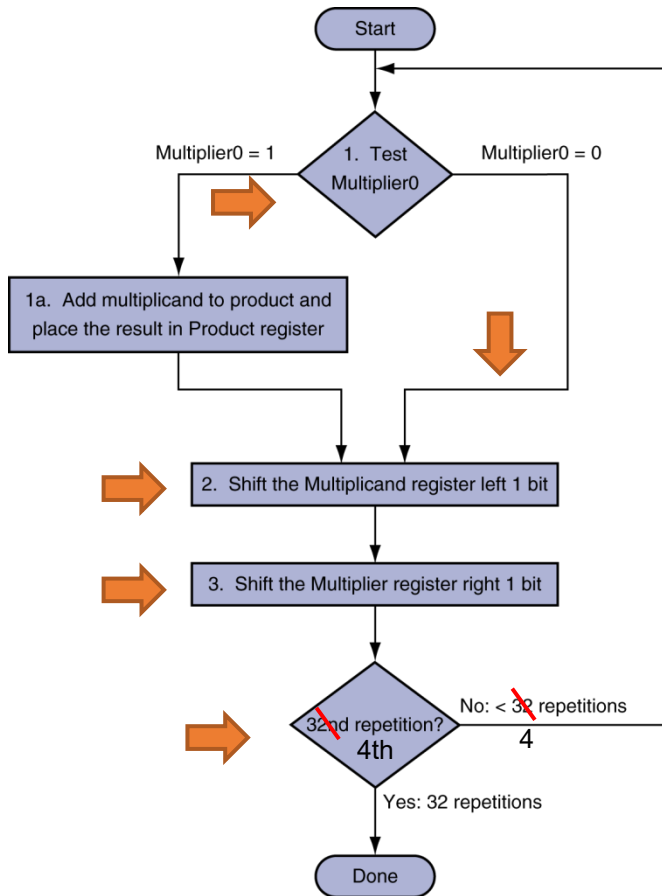
Multiplication Example, 1000 x 1001 – Iteration 2



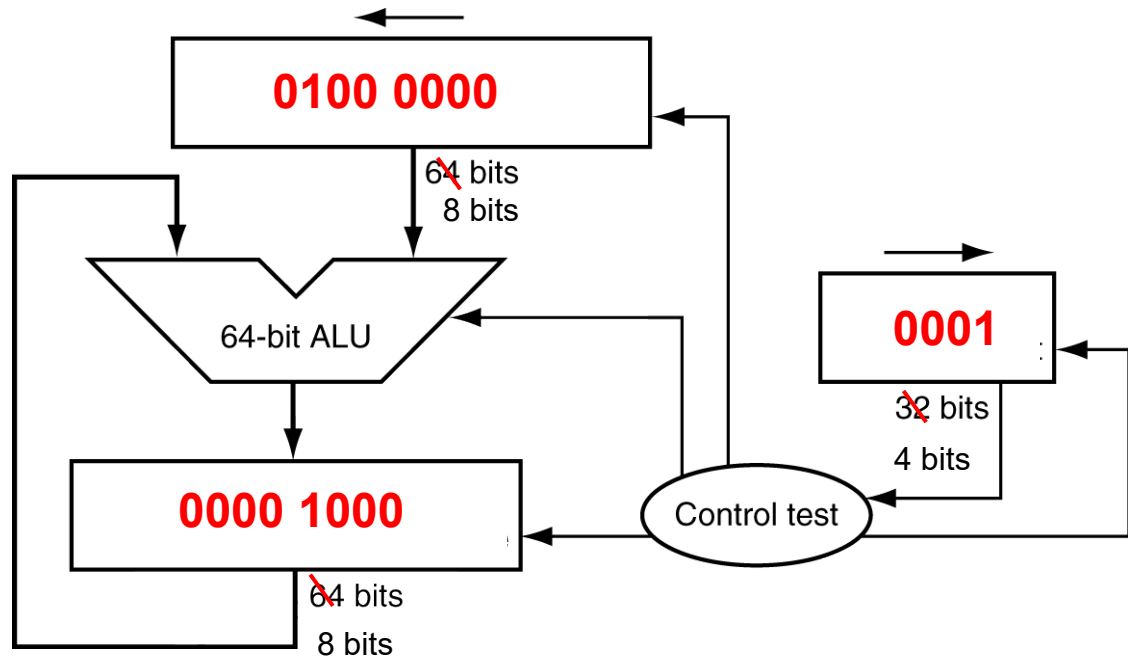
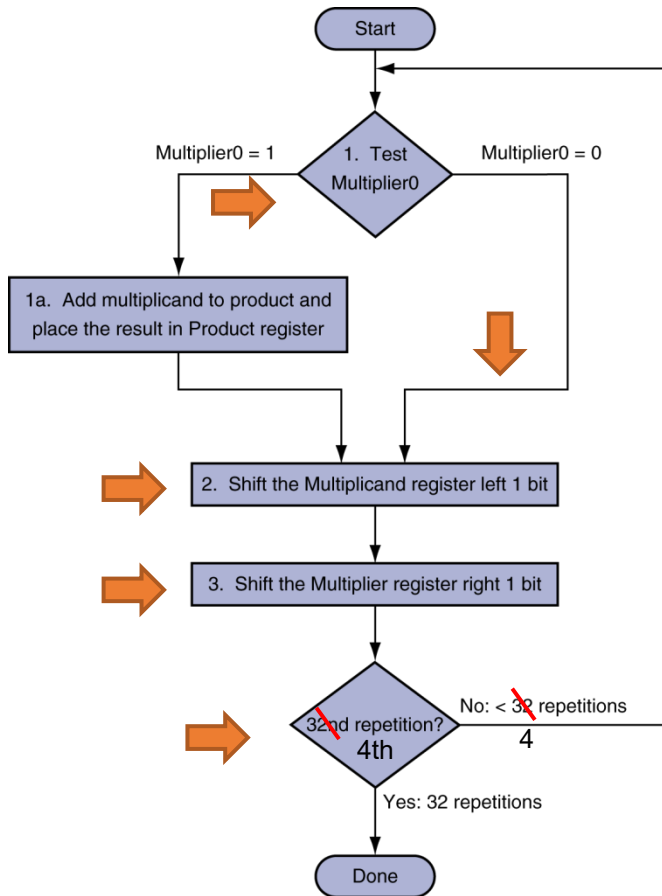
Multiplication Example, 1000 x 1001 – Iteration 3



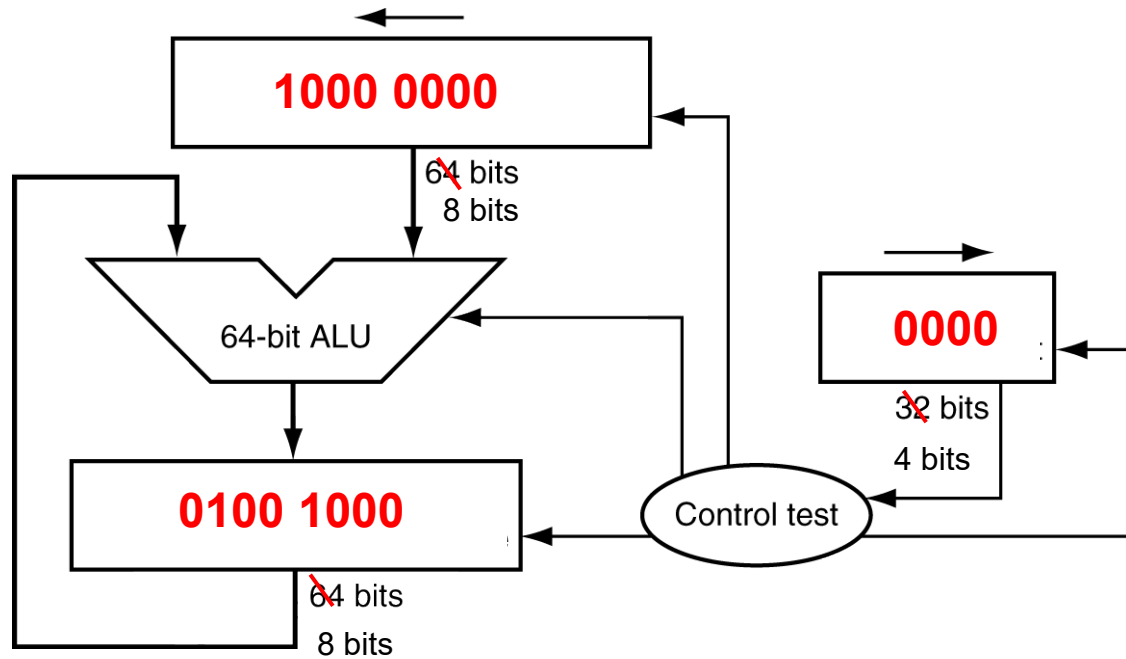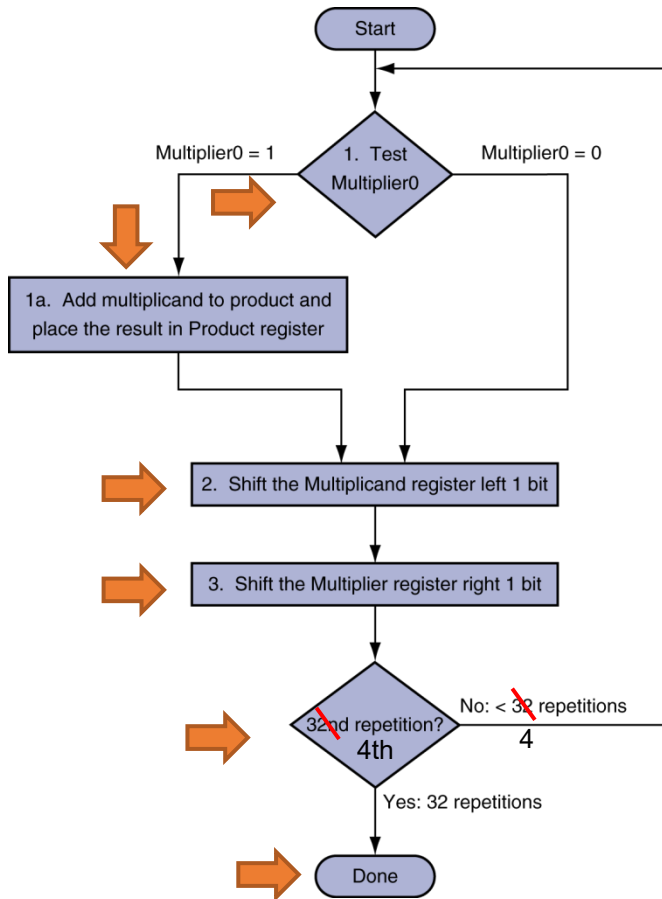Multiplication Example, 1000 x 1001 – Iteration 4




Multiplication Hardware - Summary

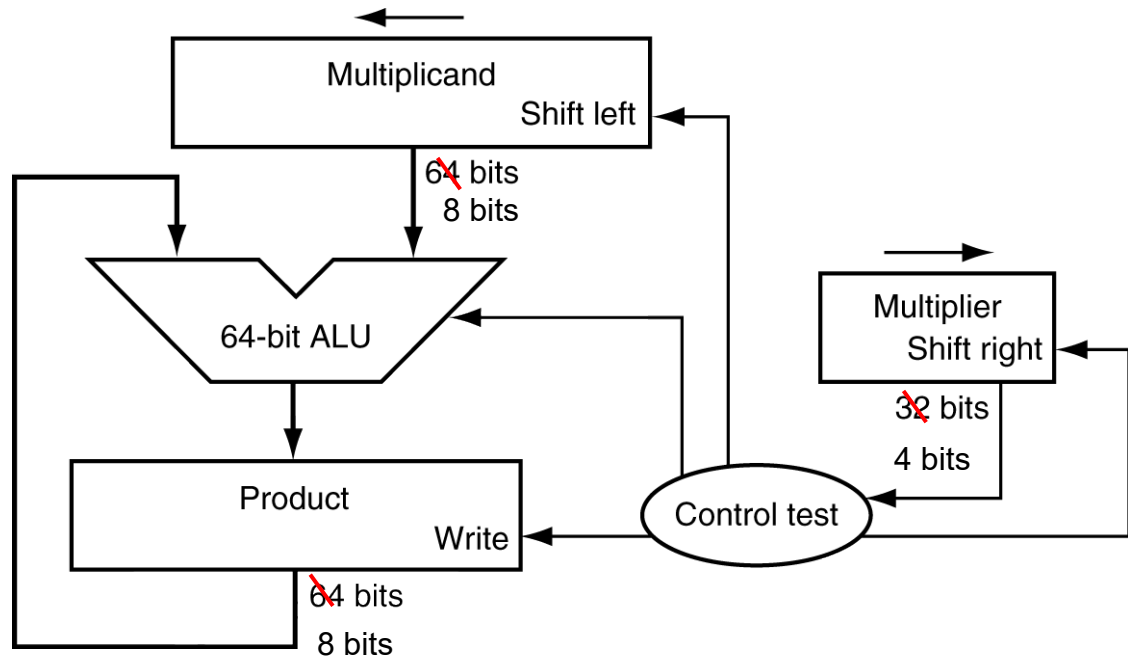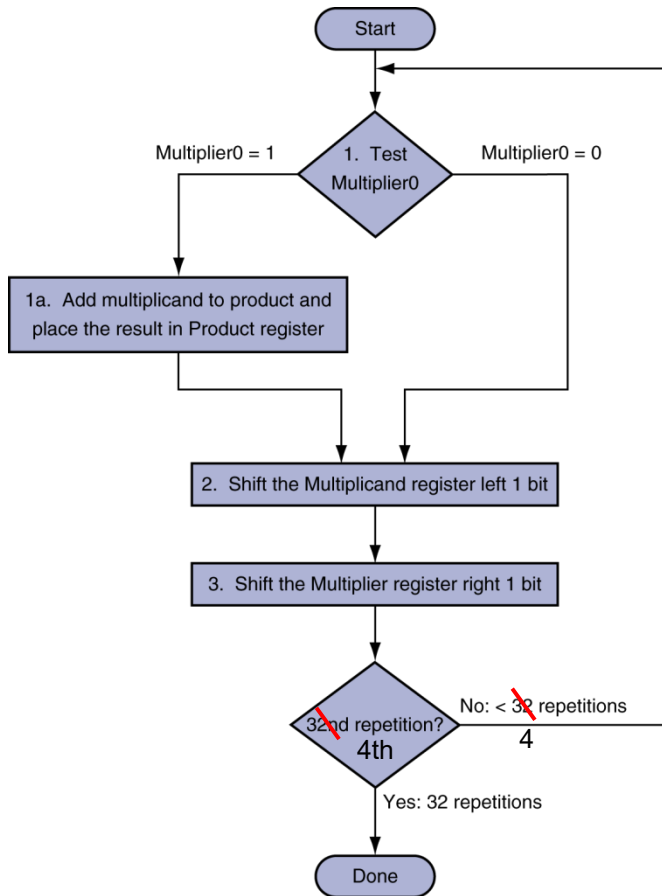


Optimized Multiplier

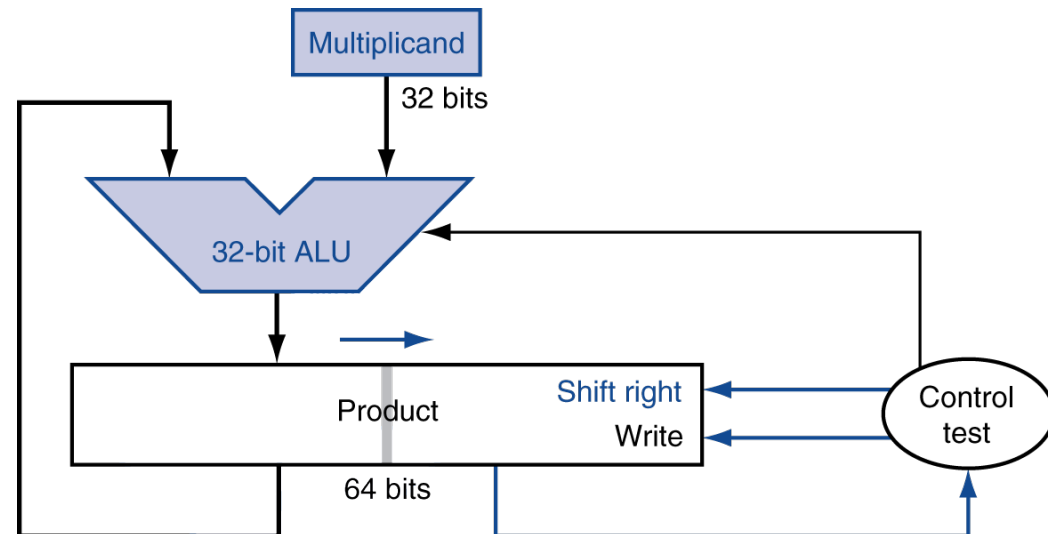- ▶ Perform steps in parallel: add/shift
 - ▶ Partial sum stored in upper 32 bits
 - ▶ Multiplier in lower 32 bits
 - ▶ Multiplier shifted out bit by bit
 - ▶ Partial sum shifts in place of multiplier
 - ▶ Do not need to extend multiplicand!
 - ▶ Everything happens in place
 - ▶ Faster, simpler hardware!




Even Faster Multiplication

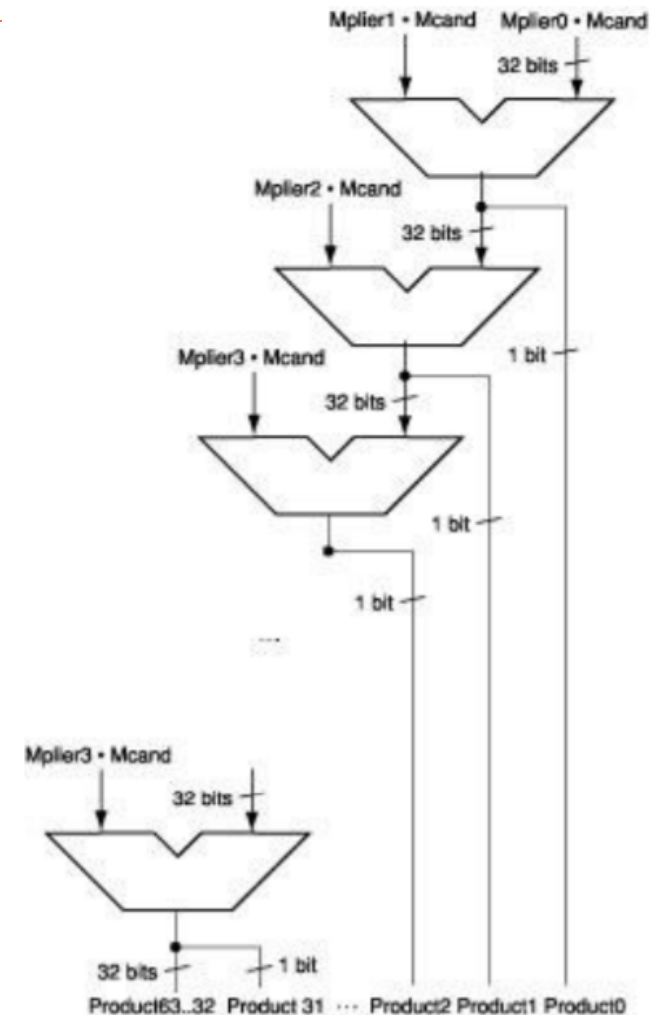- ▶ Unroll the addition “loop” and associated shifting
- ▶ Use 32 32-bit adders
 - ▶ Left input is multiplicand times a bit in multiplier
- ▶ Each adder produces 32-bits and a carry-out
 - ▶ The least significant bit of each intermediate sum is a bit of the product.
 - ▶ The other 31 bits and the carry-out are passed along as the right input to the next adder.




Faster Multiplication

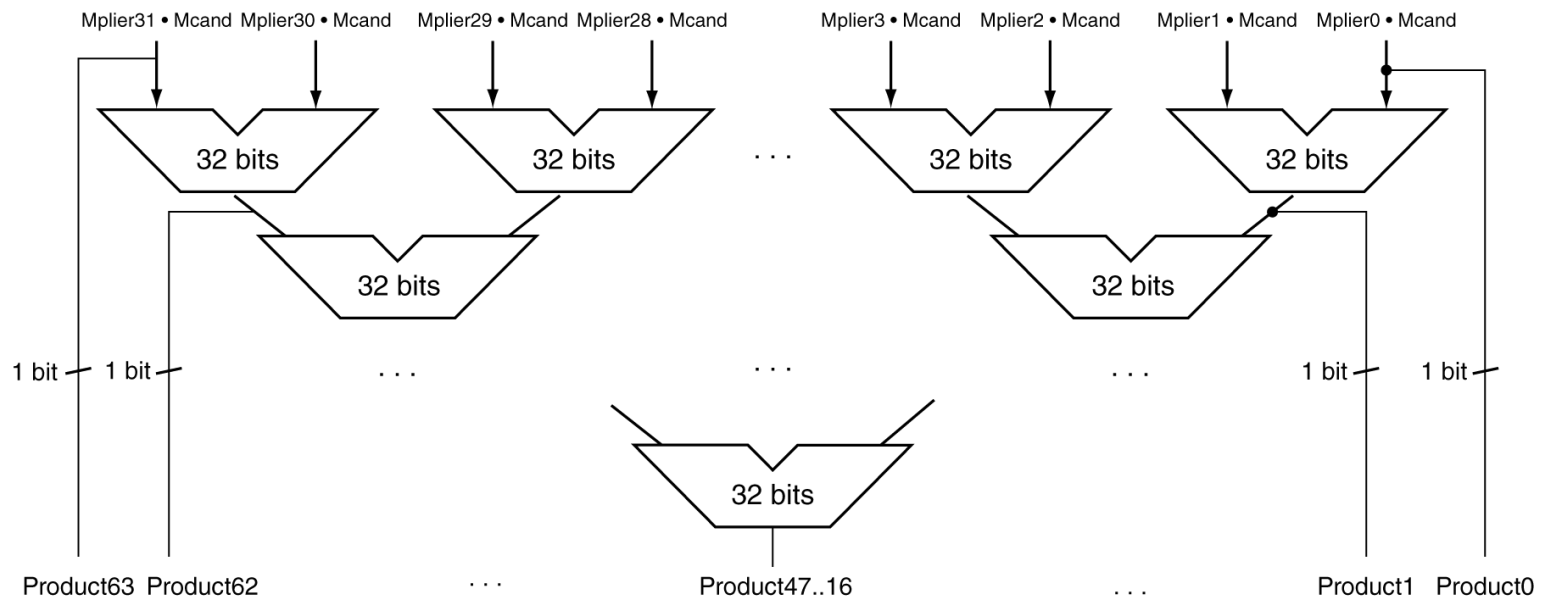- ▶ Uses multiple adders
- ▶ Several additions performed in parallel
- ▶ Takes $\log_2(32)$ or 5 add cycles



Division



Division Algorithm from Grammar school

 

Basic Division algorithm

- ▶ Line up dividend and divisor from left side
- ▶ Let remainder be leading bits of dividend
- ▶ [LOOP]
 - ▶ If remainder \geq divisor
 - Set 1 bit in quotient, subtract divisor from remainder
 - ▶ Otherwise
 - Set 0 bit in quotient,
 - ▶ Bring down next dividend bit to remainder
 - If no more bit, done
 - Jump back to [LOOP]

Division Hardware

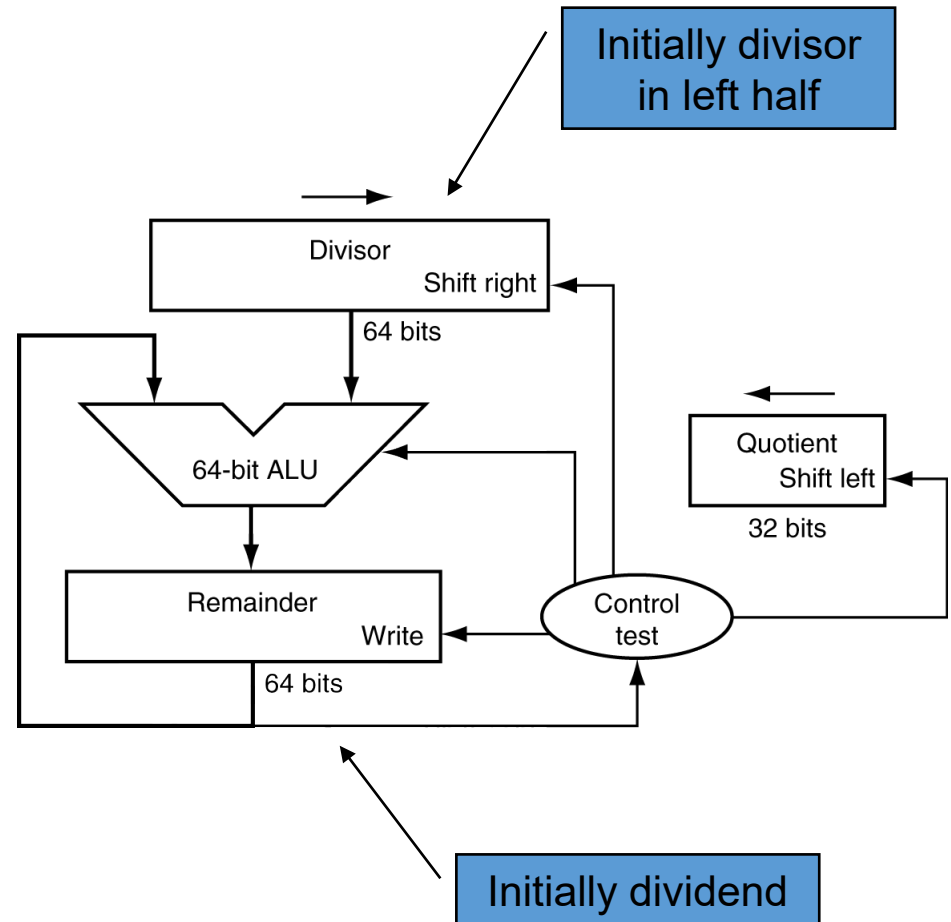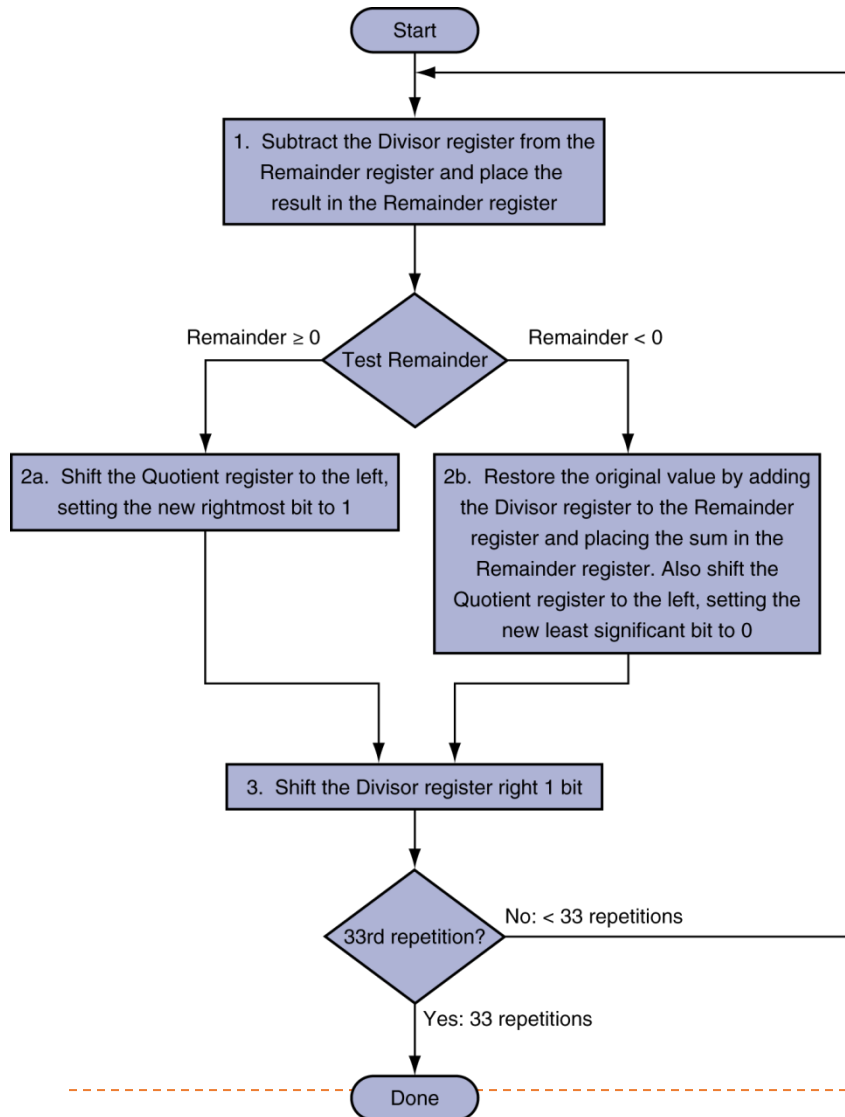

Example – 4-bit Division

- ▶ Dividend = 13 (1101_2)
- ▶ Divisor = 2 (0010_2)

dividend →

					← quotient
				•	
		<hr/>			
10)	1101	← remainder		
		1			

Division Example

- ▶ Dividend = 13 (1101_2)
- ▶ Divisor = 2 (0010_2)

Dividend →

$$\begin{array}{r} \overline{01} \\ 10 \,) \, 1101 \\ \underline{1} \\ 11 \\ \underline{-10} \\ 1 \end{array}$$

← quotient

← reminder

Division Example

- ▶ Dividend = 13 (1101_2)
- ▶ Divisor = 2 (0010_2)

Dividend →

$$\begin{array}{r} \overline{01} \\ 10 \,) \, 1101 \\ \underline{1} \\ 11 \quad \leftarrow \text{remainder} \\ \underline{-10} \\ 10 \end{array}$$

← quotient

Division Example

- ▶ Dividend = 13 (1101_2)
- ▶ Divisor = 2 (0010_2)

Dividend →

$$\begin{array}{r} \text{← quotient} \\ 011 \text{ .} \\ \hline 10 \) \ 1101 \\ \underline{1} \\ 11 \\ \underline{-10} \\ 10 \text{ ← remainder} \\ \underline{-10} \\ 0 \end{array}$$

Division Example

- ▶ Dividend = 13 (1101_2)
- ▶ Divisor = 2 (0010_2)

Dividend →

$$\begin{array}{r} \text{← quotient} \\ \overline{011} . \\ 10 \) \ 1101 \\ \underline{1} \\ 11 \\ \underline{-10} \\ 10 \text{ ← remainder} \\ \underline{-10} \\ 01 \end{array}$$



Division Example

- ▶ Dividend = 13 (1101_2)
- ▶ Divisor = 2 (0010_2)



Dividend →

					← quotient
				<u>0110</u>	.
10)	1101			
		1			
		11			
		<u>-10</u>			
		10			← remainder
		<u>-10</u>			
		01			

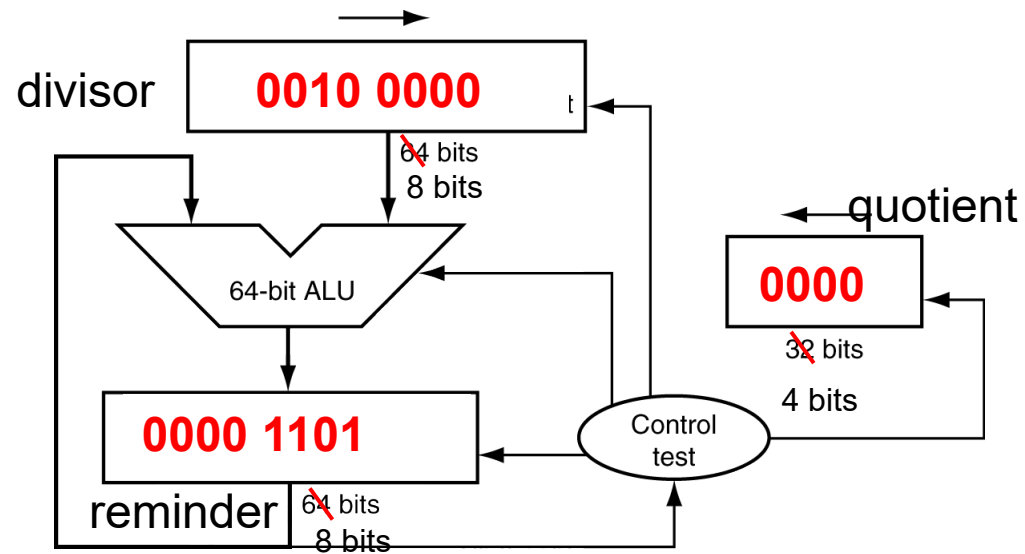
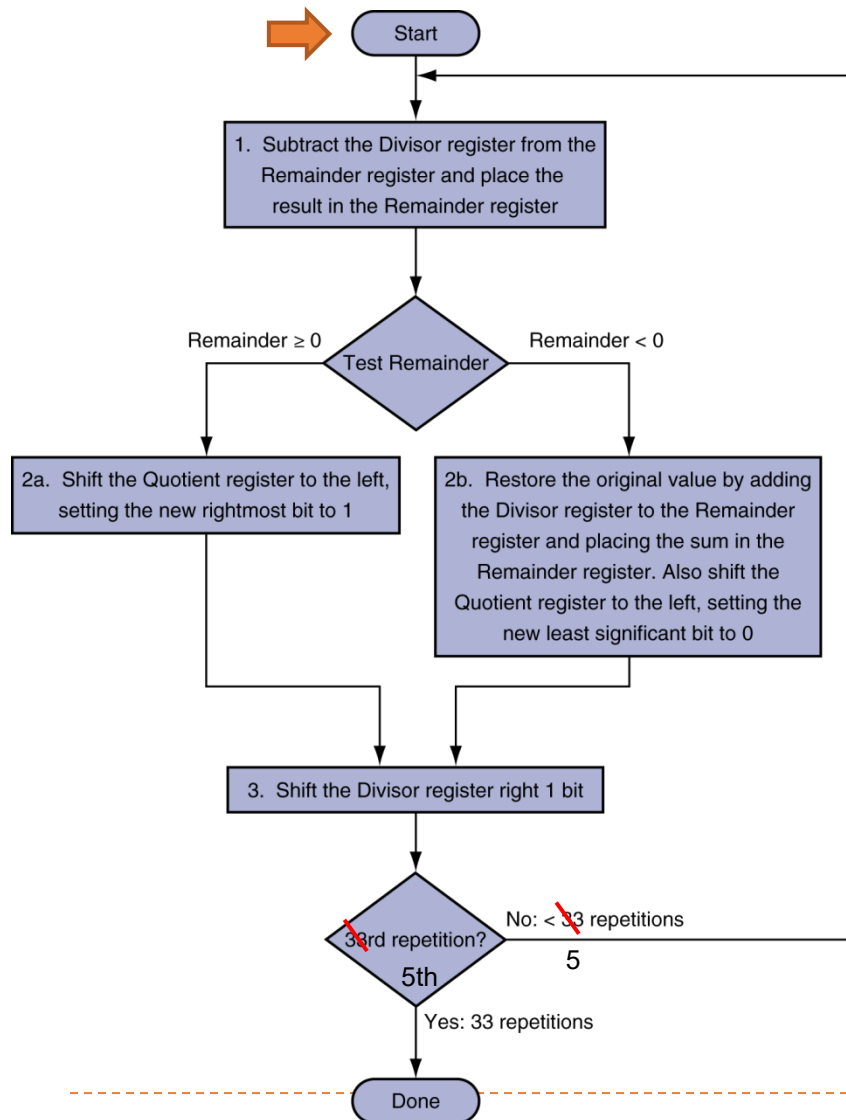
Division Example $1101_2 / 0010_2$ – start





Division Example – Iteration 1

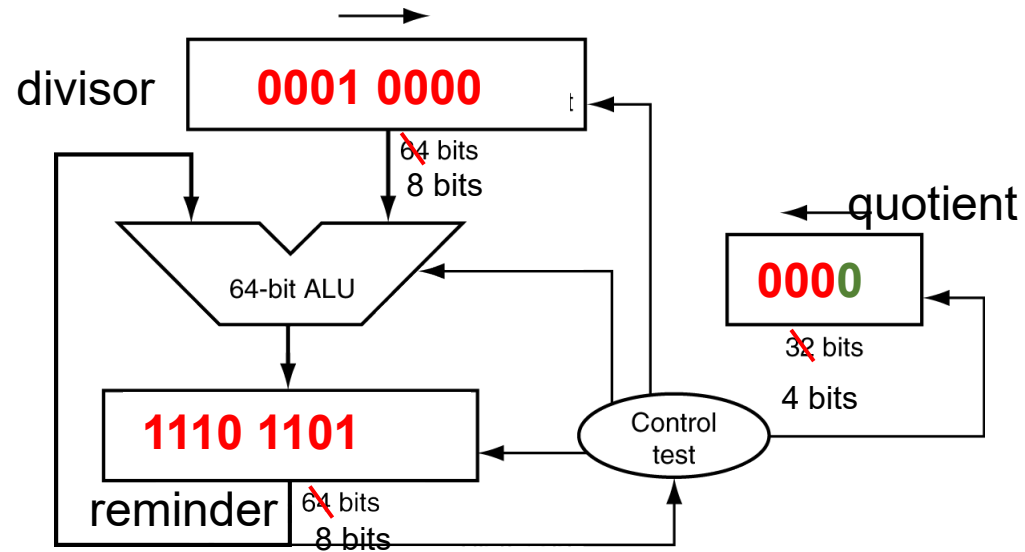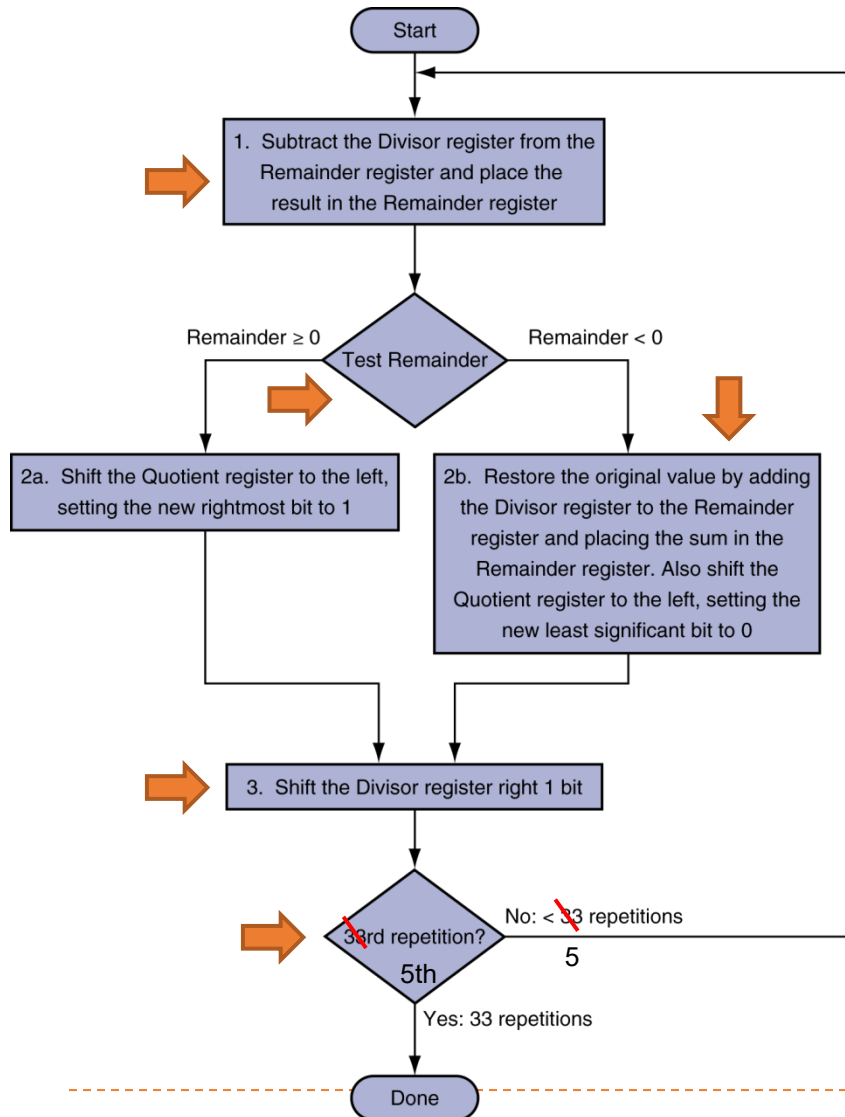



Division Example – Iteration 2

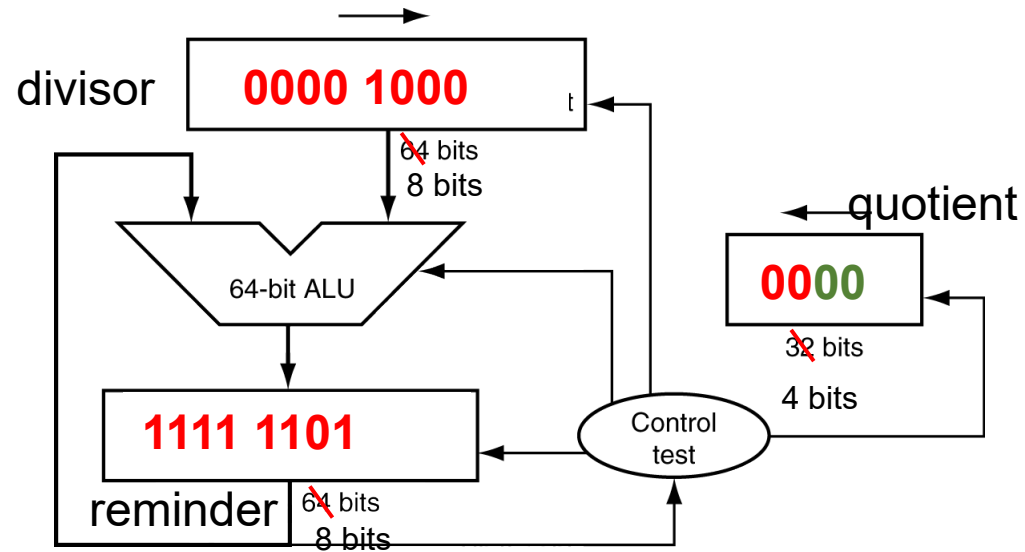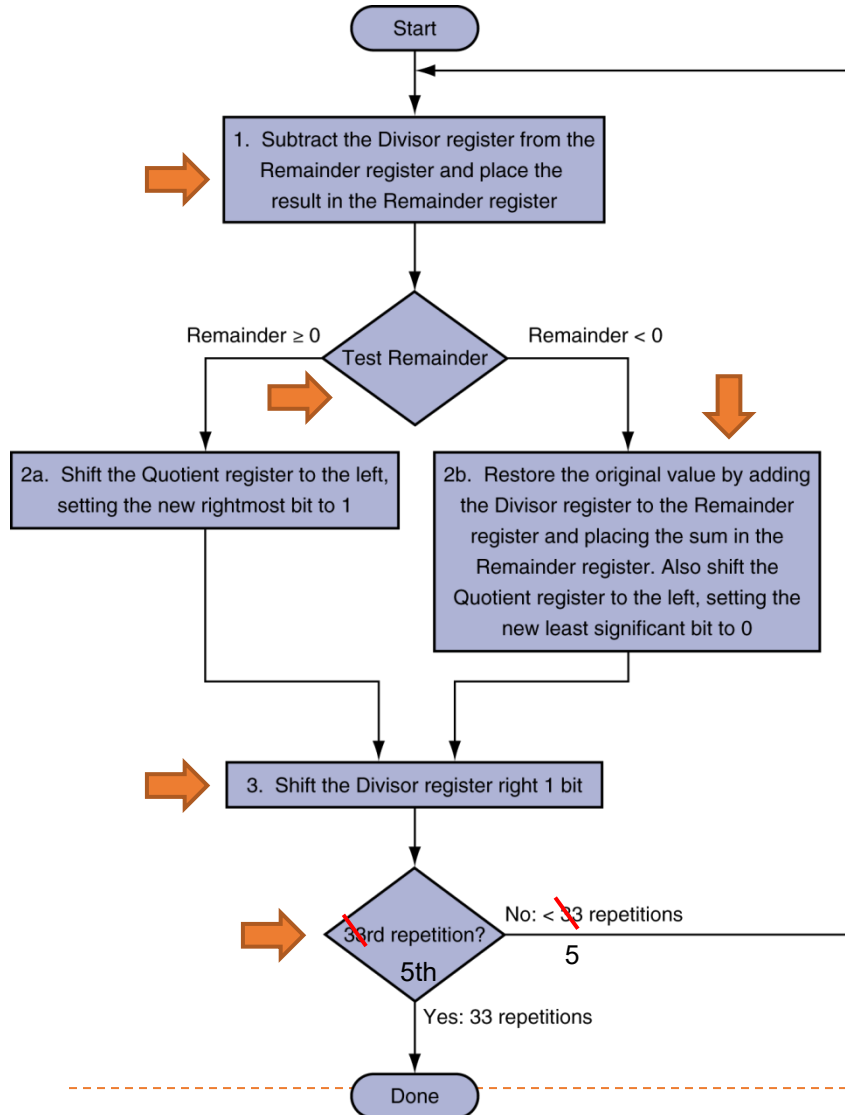



Division Example – Iteration 3

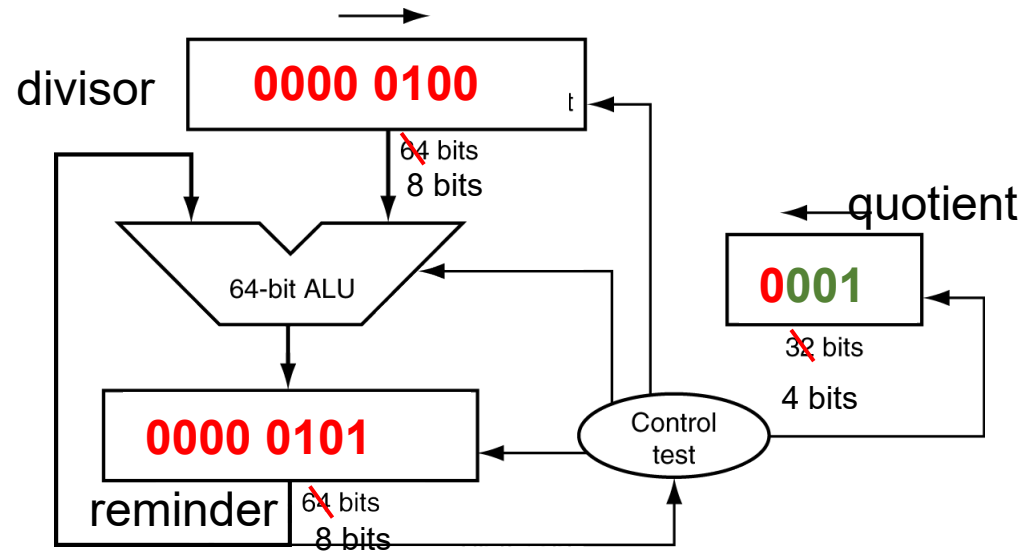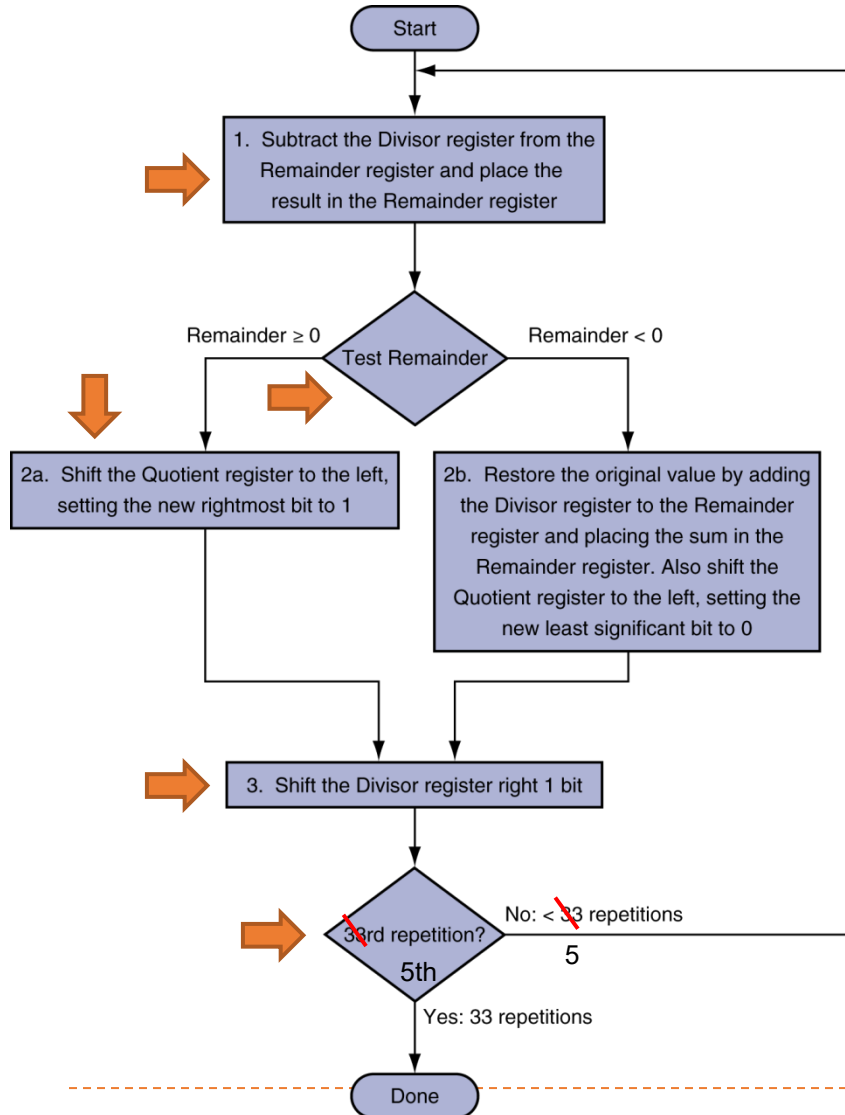



Division Example – Iteration 4

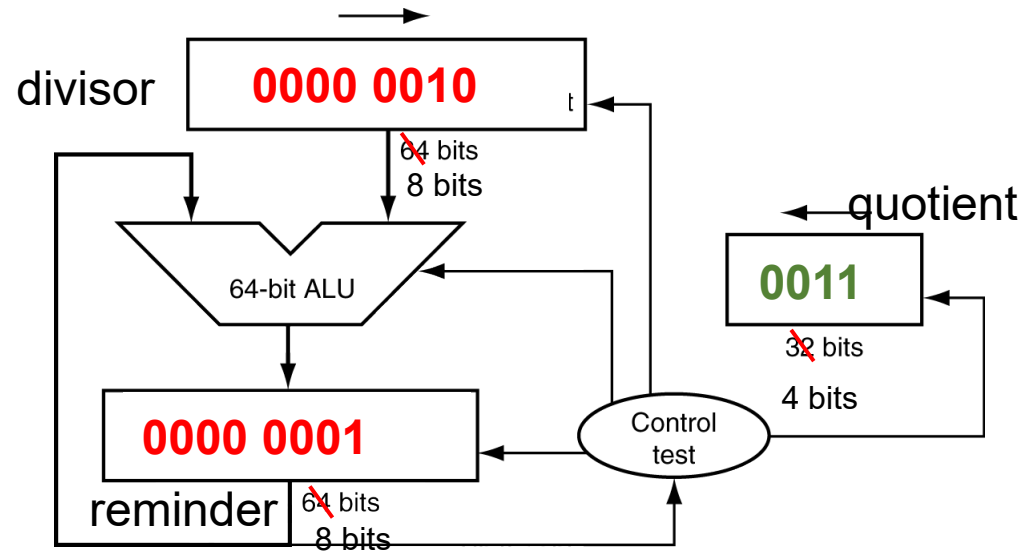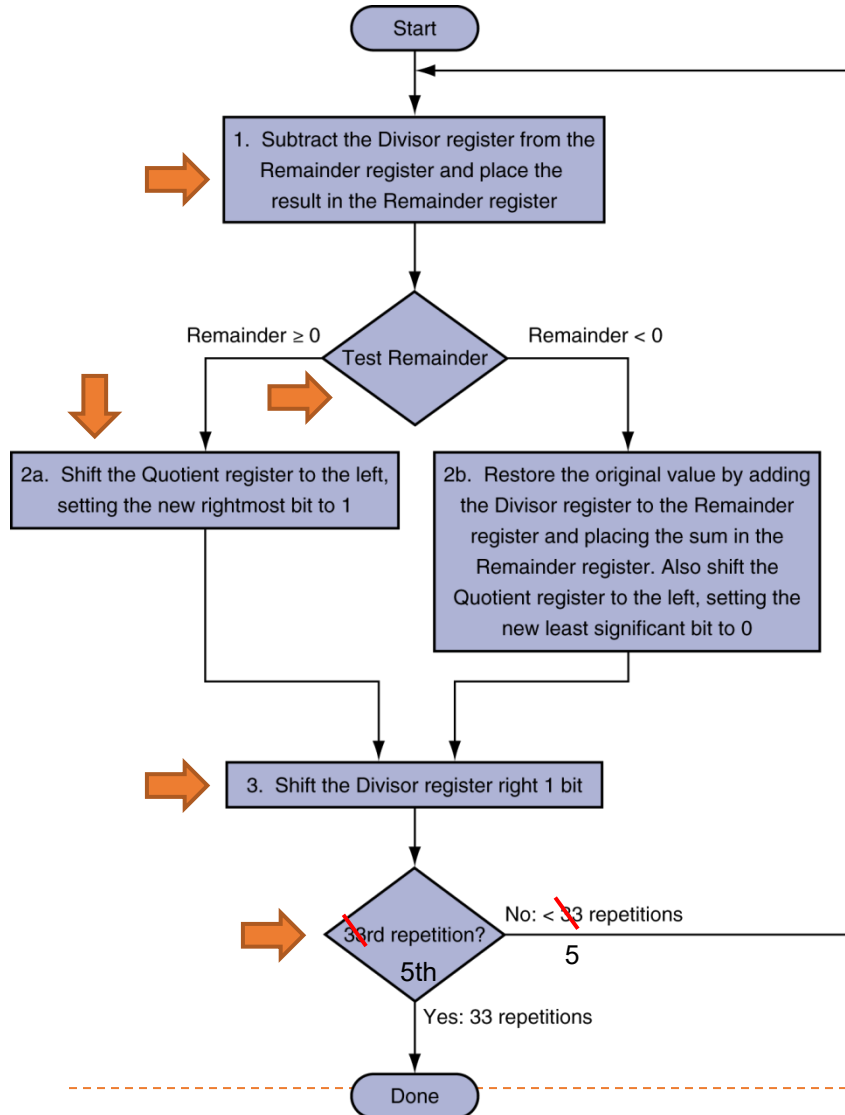

Division Example – Iteration 5

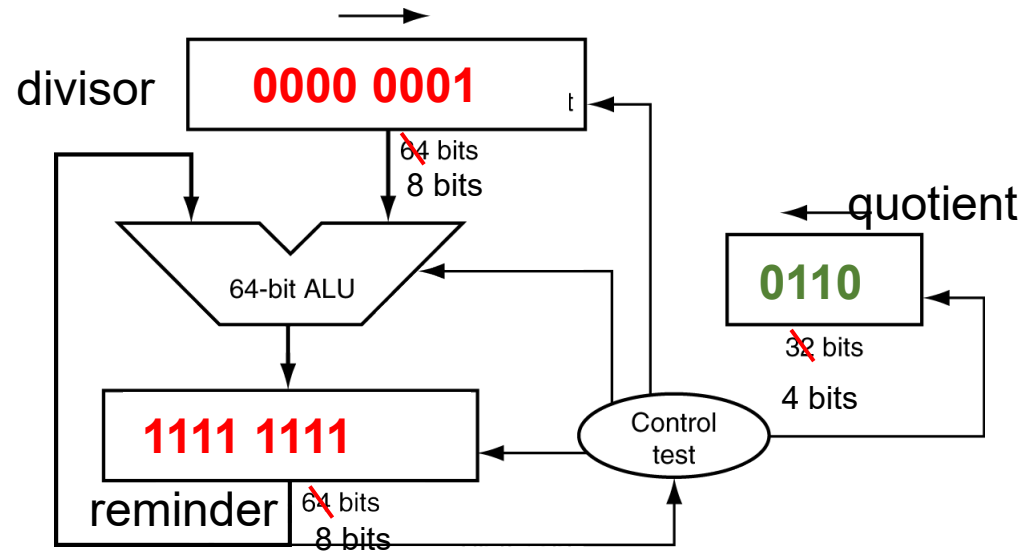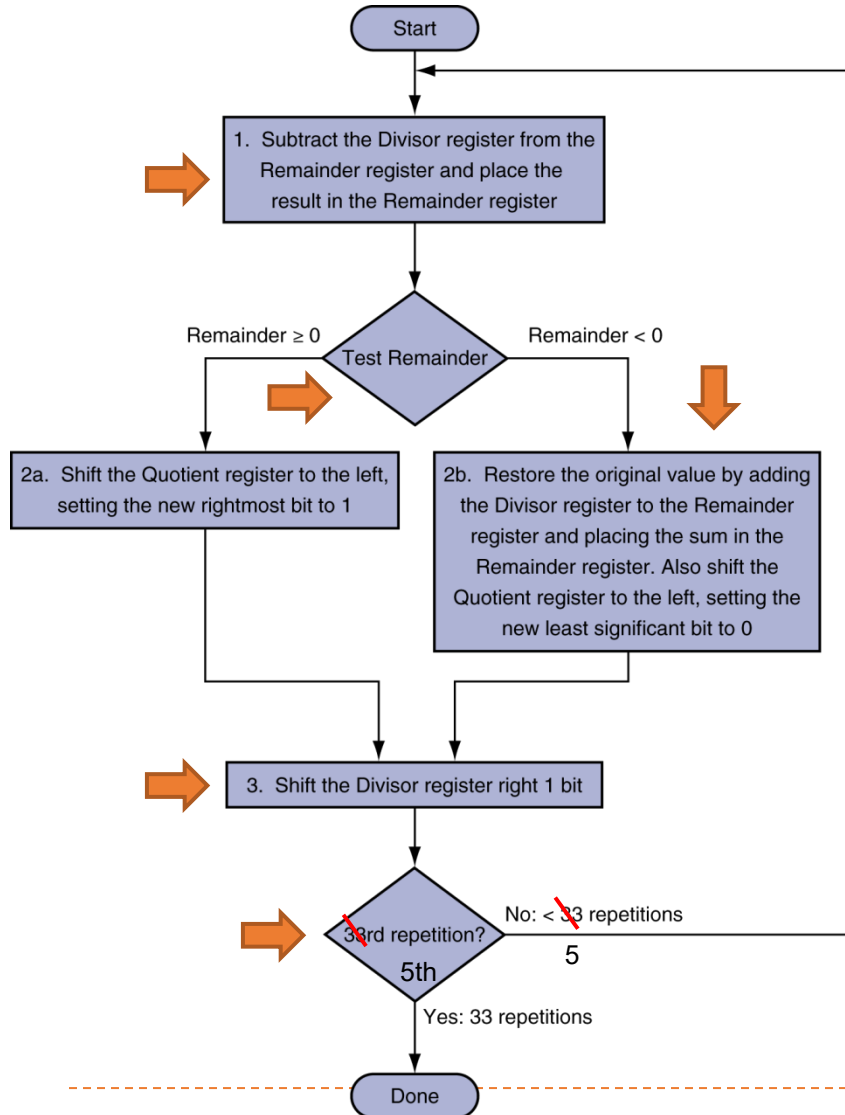


Division Example – Done

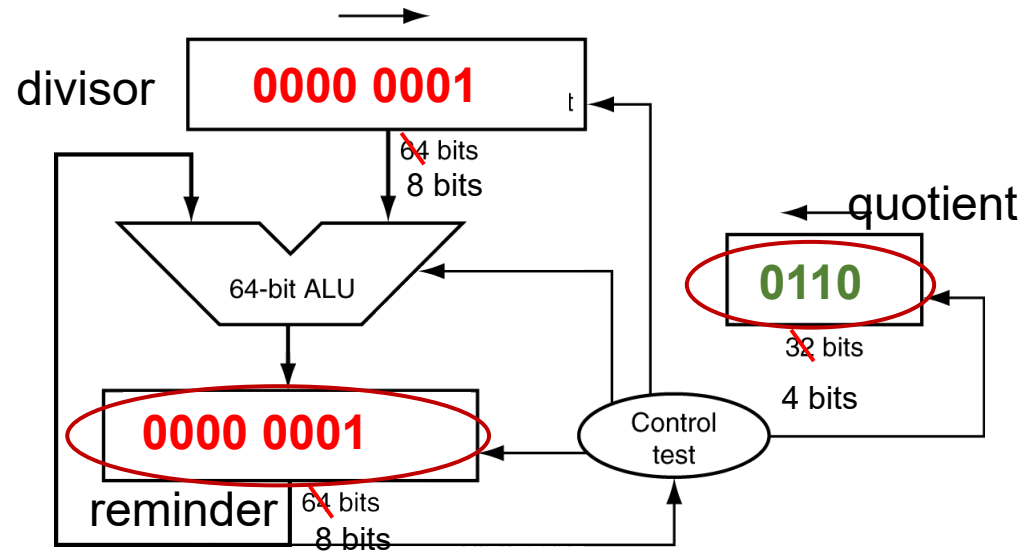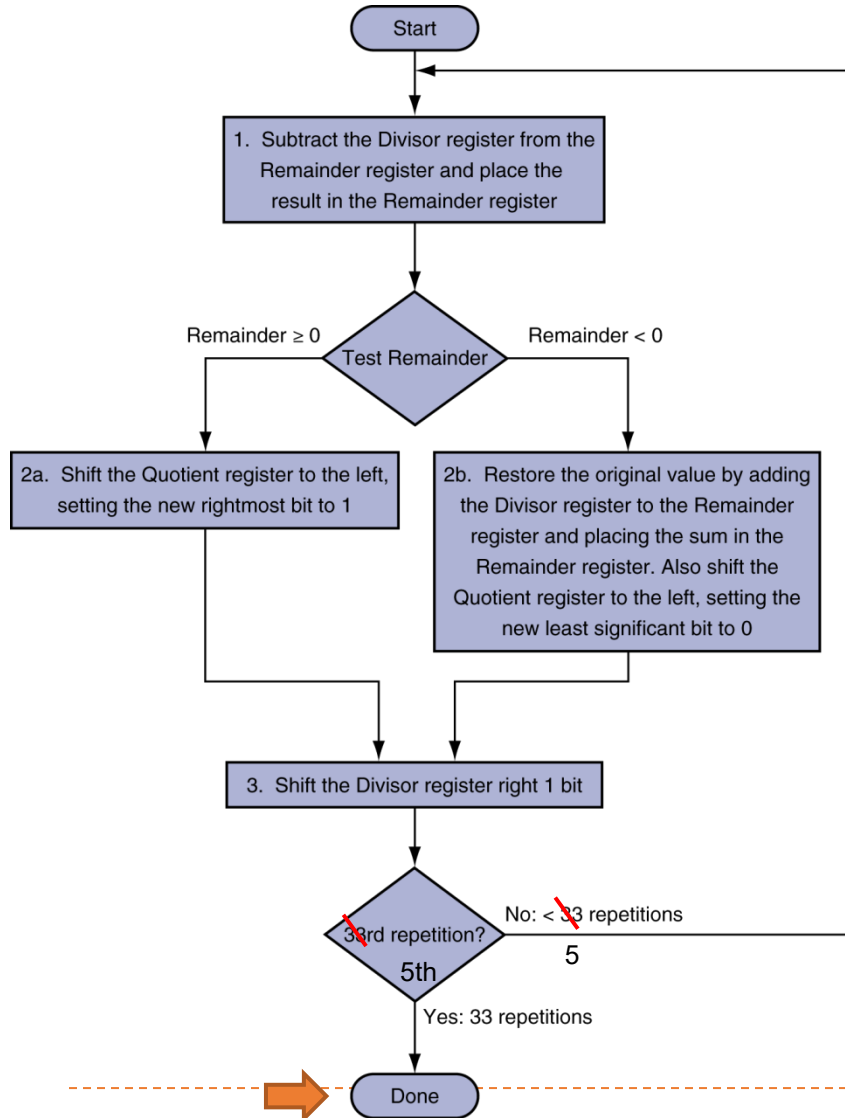


Q: Can we do better?

An Improved Version

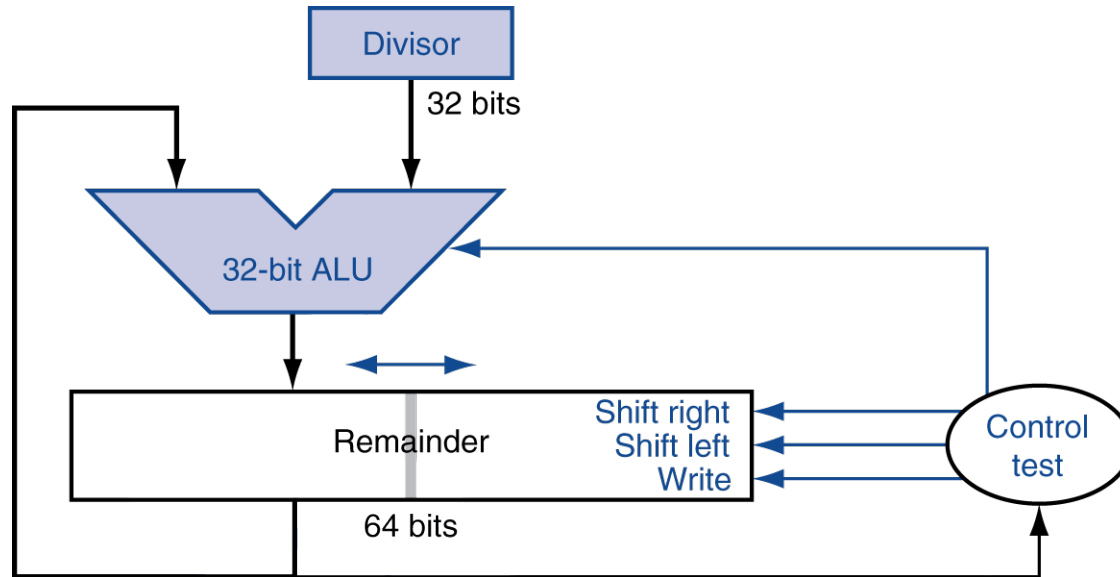

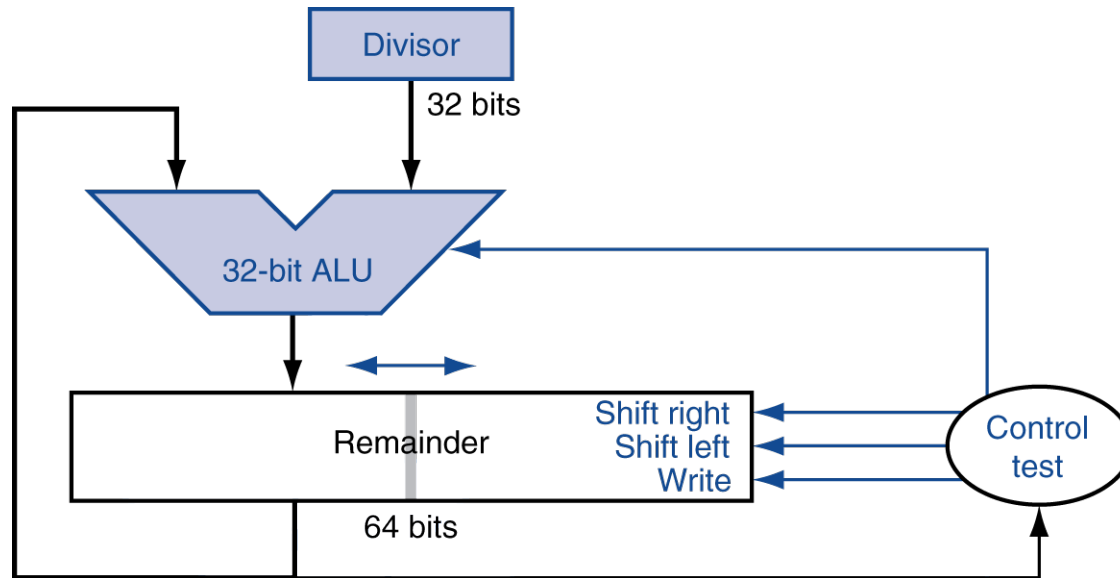- ▶ Initially, dividend is put into lower 32bit of Remainder
- ▶ For each iteration
 - ▶ Subtraction and possible restore to Remainder
 - ▶ Remainder shift 1 bit to the left
 - ▶ Quotient bit is stored to right side of Remainder
- ▶ At the end, top 32bit is remainder, lower 32bit is quotient



- ▶ Looks a lot like a multiplier!
 - ▶ Same hardware can be used for both
-

Faster Division

- ▶ Can't use parallel hardware as in multiplication
 - ▶ Subtraction is conditional on sign of remainder
- ▶ Faster dividers (e.g. SRT division) generate multiple quotient bits per step
 - ▶ Still require multiple steps

RISC-V M Extension

1. `mul` performs a 32 x 32 register multiply and stores the lower 32 bits of the 64-bit result in a register.
 2. `mulh` and `mulhu` perform signed and unsigned register multiply, respectively, and store the upper 32 bits of the 64-bit result in a register.
 3. `mulhsu` performs a signed x unsigned register multiply and stores the upper 32 bits of the 64-bit result in a register.
 4. `div` and `divu` perform signed and unsigned 32/32 register division
 5. `rem` and `remu` perform signed and unsigned 32%32 remainder
-

Reference Readings

- ▶ Patterson, "Computer Organization And Design"
 - ▶ A.2, A.3, 3.3, 3.4
 - ▶ Tanenbaum, "Structured Computer Organization"
 - ▶ Sec 3.2
 - ▶ Bryant, "Computer Systems"
 - ▶ Sec 4.2.2 – 4.2.4
-